

EECS 370 - Lecture 11

Single & Multi-Cycle Data Path




Announcements

- P2
 - Three parts: part a is due **Thursday**
- HW 2
 - Posted on website, due next **Mon**
- Lab due Wed @ 11:55 pm
 - Lab meets Fr/M before exam, not after exam
- Midterm exam **Wed 7-9 pm**
 - Sample exams on website
 - You can bring 1 sheet (double sided is fine) of notes
 - We will provide LC2K encodings + ARM cheat sheet
 - Calculator that doesn't connect to internet is recommended

Hybrid OH

- Looking for extra help?
- Want shorter wait times?
- Hybrid OH: Tu/Th 5-6 in DOW 1017
 - Get individual help from student staff
 - Professor will handle group questions while you wait
 - Have only had ~4 students at a time so far


Implementing an FSM

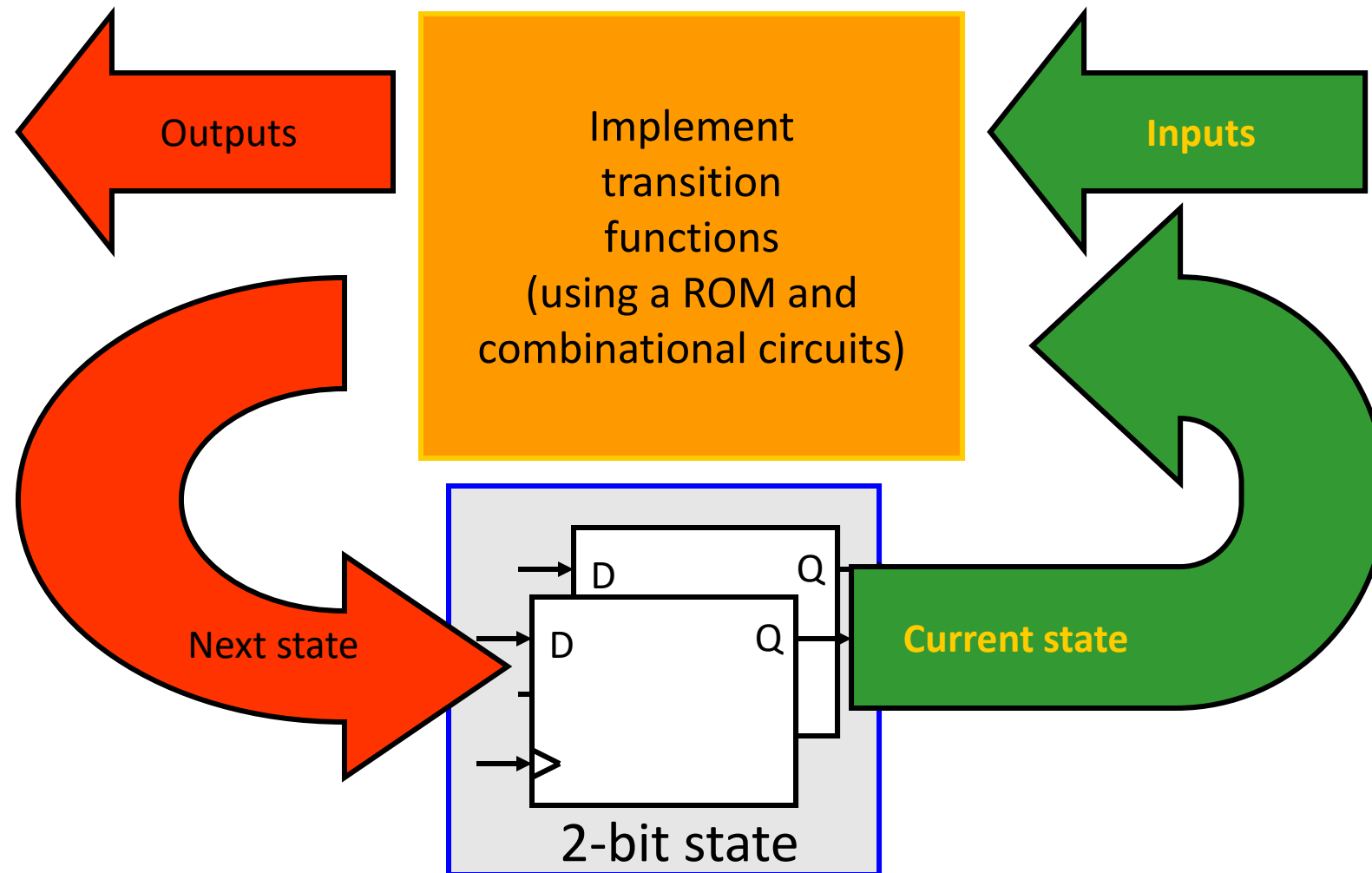

8-entry 4-bit ROM

Input	Output
000	1001
001	0100
010	0010
011	1001
100	0010
101	0001
110	1000
111	0000


This ROM
corresponds to this
truth table

 

Implementing Combinational Logic

- Custom logic
 - Pros:
 - Can optimize the number of gates used
 - Cons:
 - Can be expensive / time consuming to make custom logic circuits
- Lookup table:
 - Pros:
 - Programmable ROMs (Read-Only Memories) are very cheap and can be programmed very quickly
 - Cons:
 - Size requirement grows exponentially with number of inputs (adding one just more bit **doubles** the storage requirements!)

Controller Design So far

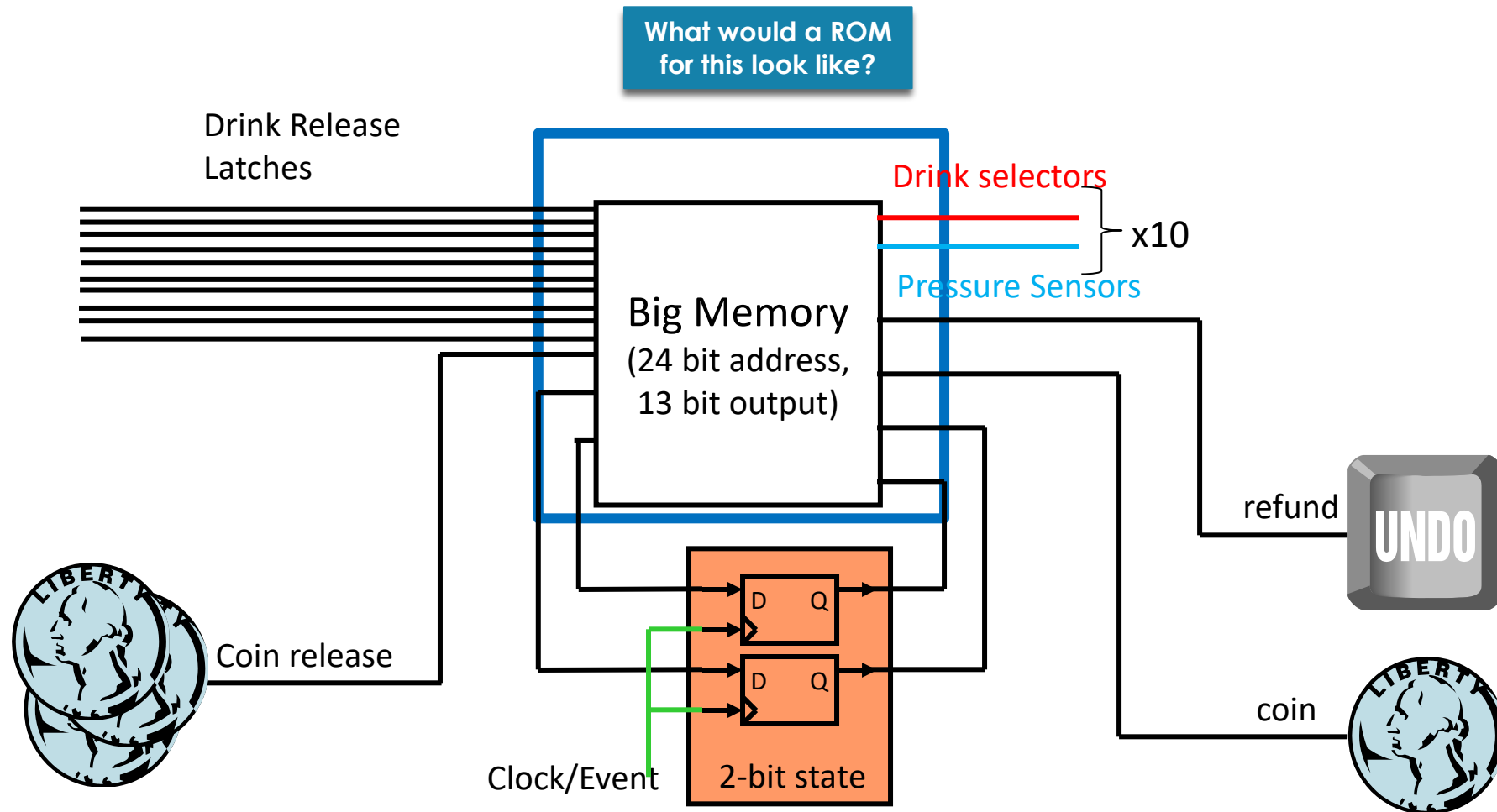

ROM for Vending Machine

Size of ROM is (# of ROM entries * size of each entry)

- # of ROM entries = $2^{\text{input_size}} = 2^{24}$
- Size of each entry = output size = 13 bits


We need 2^{24} entry, 13 bit ROM memories

- **218,103,808 bits of ROM (26 MB)**
- Biggest ROM I could find on Jameco was 4 MB @ \$6
 - Need 7 of these at \$42??
- Let's see if we can do better

Reducing the ROM needed

- Idea: let's do a hybrid between combinational logic and a lookup table
 - Use basic hardware (AND / OR) gates where we can, and a ROM for everything more complicated
 - AND / OR gates are mass producible & cheap!
 - ~\$0.15 each on Jameco

IC 74HC08 QUAD 2-INPUT POSITIVE AND GATE

 

[View larger image](#)

Jameco Part no.: 45225
Manufacturer: [Major Brands](#)
Manufacturer p/n: 74HC08
HTS code: 8542390000
[Fairchild Semiconductors](#) [83 KB]
[Data Sheet \(current\)](#) [83 KB]
Representative Datasheet, MFG may vary

\$0.49 ea

1,061 In Stock
More Available - 7 weeks

Qty

1


Add to cart

[+ Add to my favorites](#)

Reducing the ROM needed

- Observation: overall logic doesn't really need to distinguish between **which** button was pressed
 - That's only relevant for choosing **which** latch is released, but overall logic is the same
- Replace 10 selector inputs and 10 pressure inputs with a **single** bit input (drink selected)
 - Use drink selection input to specify which drink release latch to activate
 - Only allow trigger if pressure sensor indicates that there is a bottle in that selection. (10 2-bit ANDs)

Putting it all together

 

Total cost of our controller

- Now:
 - 2 current state bits + 3 input bits (5 bit ROM address)
 - 2 next state bits + 2 control trigger bits (4 bit memory)
 - $2^5 \times 4 = 128$ bit ROM
 - 1-millionth size of our 26 MB ROM 🤖
- Total cost on Jameco:
 - Flip-flops to store state: \$3
 - ROM to implement logic: \$3
 - AND/OR gates: \$5
 - **Total: \$11**
- Could probably do a lot cheaper if we buy in bulk


Agenda

- FSM Implementation
- ROMs
- Making our FSM more efficient
- **Single Cycle Processor Design Overview**
- Supporting each instruction
 - ADD / NOR
 - LW / SW
 - BEQ
 - JALR


Single-Cycle Processor Design

- General-Purpose Processor Design
 - Fetch Instructions
 - Decode Instructions
 - Instructions are input to control ROM
 - ROM data controls movement of data
 - Incrementing PC, reading registers, ALU control
 - Clock drives it all
 - Single-cycle datapath: Each instruction completes in one clock cycle

LC2K Datapath Implementation

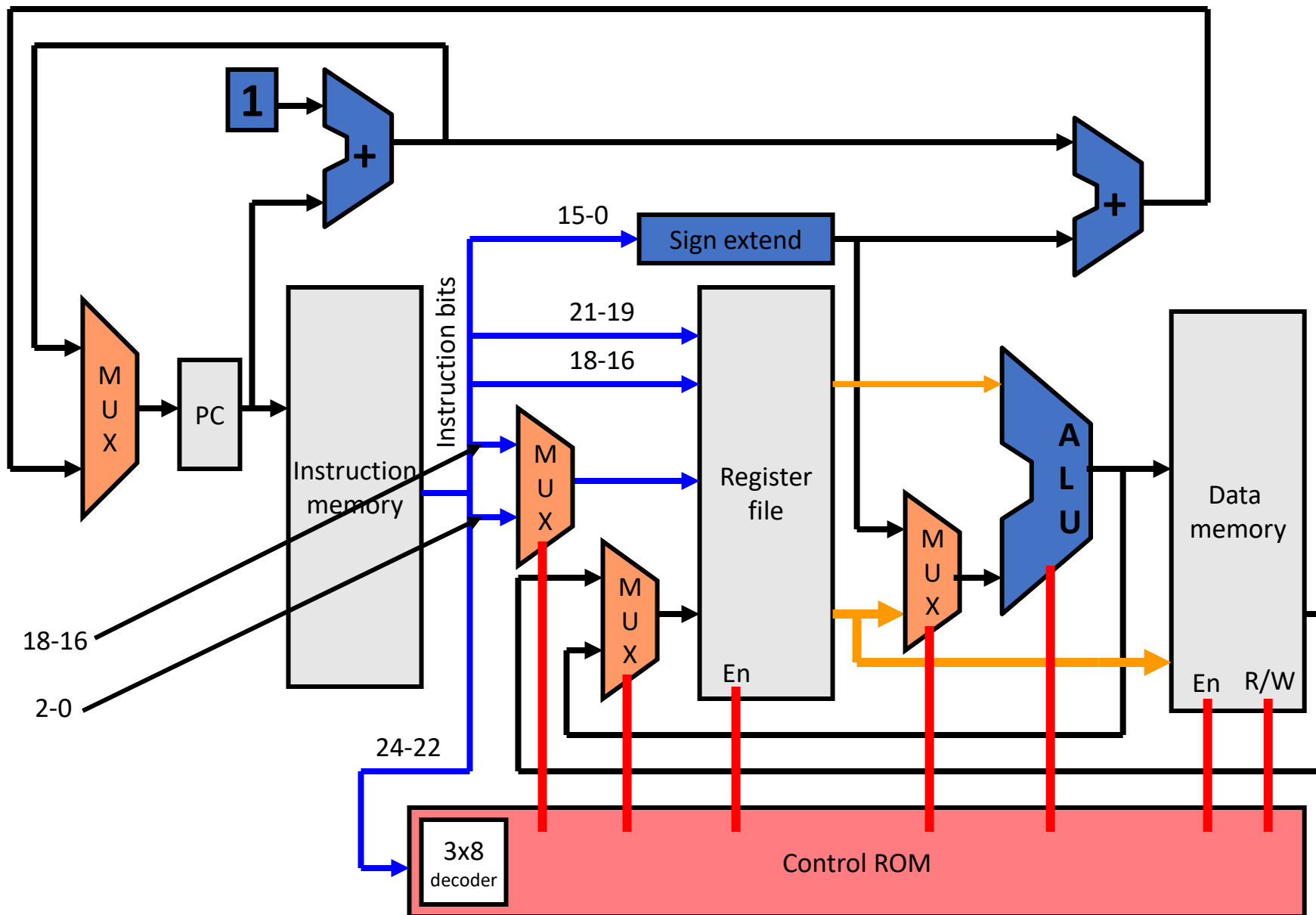


Building Blocks for the LC2K

 

Here are the pieces, go build yourself a processor!


Control Building Blocks (1)

 

Connect one of the inputs to OUT based on the value of select

If (! select)
 OUT = IN1
Else
 OUT = IN2

Control Building Blocks (2)

 


Decoder activates one of the output lines based on the input

IN	OUT
<u>210</u>	<u>76543210</u>
000	00000001
001	00000010
010	00000100
011	00001000
etc.	

ROM stores preset data in each location

- Give address, get data.

Compute Building Blocks (1)

 

Perform basic arithmetic functions

$$\text{OUT} = f(\text{IN1}, \text{IN2})$$

$$\text{EQ} = (\text{IN1} == \text{IN2})$$

For LC2K:


f=0 is add

f=1 is nor

For other processors, there are many more functions.

Just adds

Compute Building Blocks (2)

 

Sign extend (SE) input by replicating the MSB to width of output


$$\text{OUT}(31:0) = \text{SE}(\text{IN}(15:0))$$

$$\text{OUT}(31:16) = \text{IN}(15)$$

$$\text{OUT}(15:0) = \text{IN}(15:0)$$

Useful when compute unit is wider than data

State Building Blocks (1)

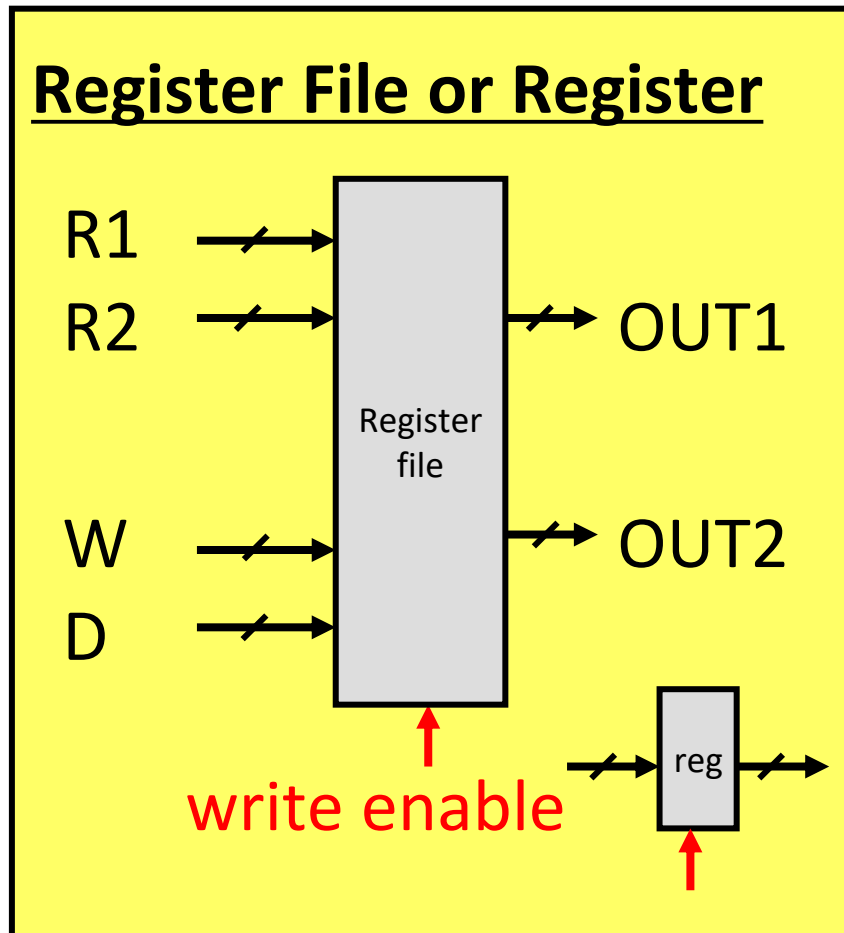

Small/fast memory to store temporary values

n entries (LC2 = 8)

r read ports (LC2 = 2)


w write ports (LC2 = 1)

* R_i specifies register number to read

* W specifies register number to write

* D specifies data to write

State Building Blocks (2)

 


Slower storage structure to hold large amounts of stuff.

Use 2 memories for LC2K


- * Instructions
- * Data
- * 65,536 total words

Recap: LC2K Instruction Formats

 
- Tells you which bit positions mean what
- R type instructions (add '000', nor '001')



 
- I type instructions (lw '010', sw '011', beq '100')



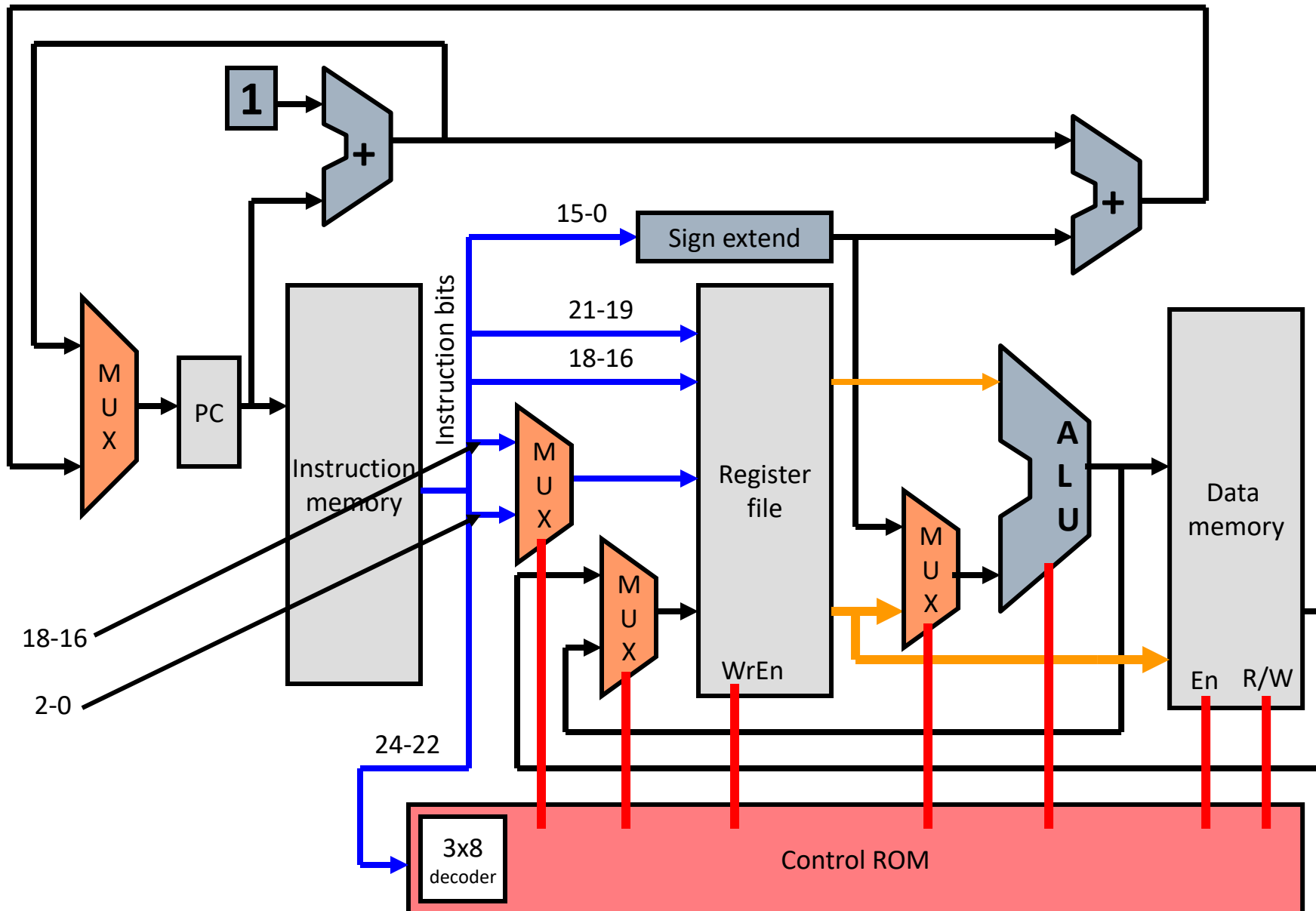
LC2K Single-Cycle Datapath Implementation



 Executing an **ADD** Instruction on LC2K Datapath




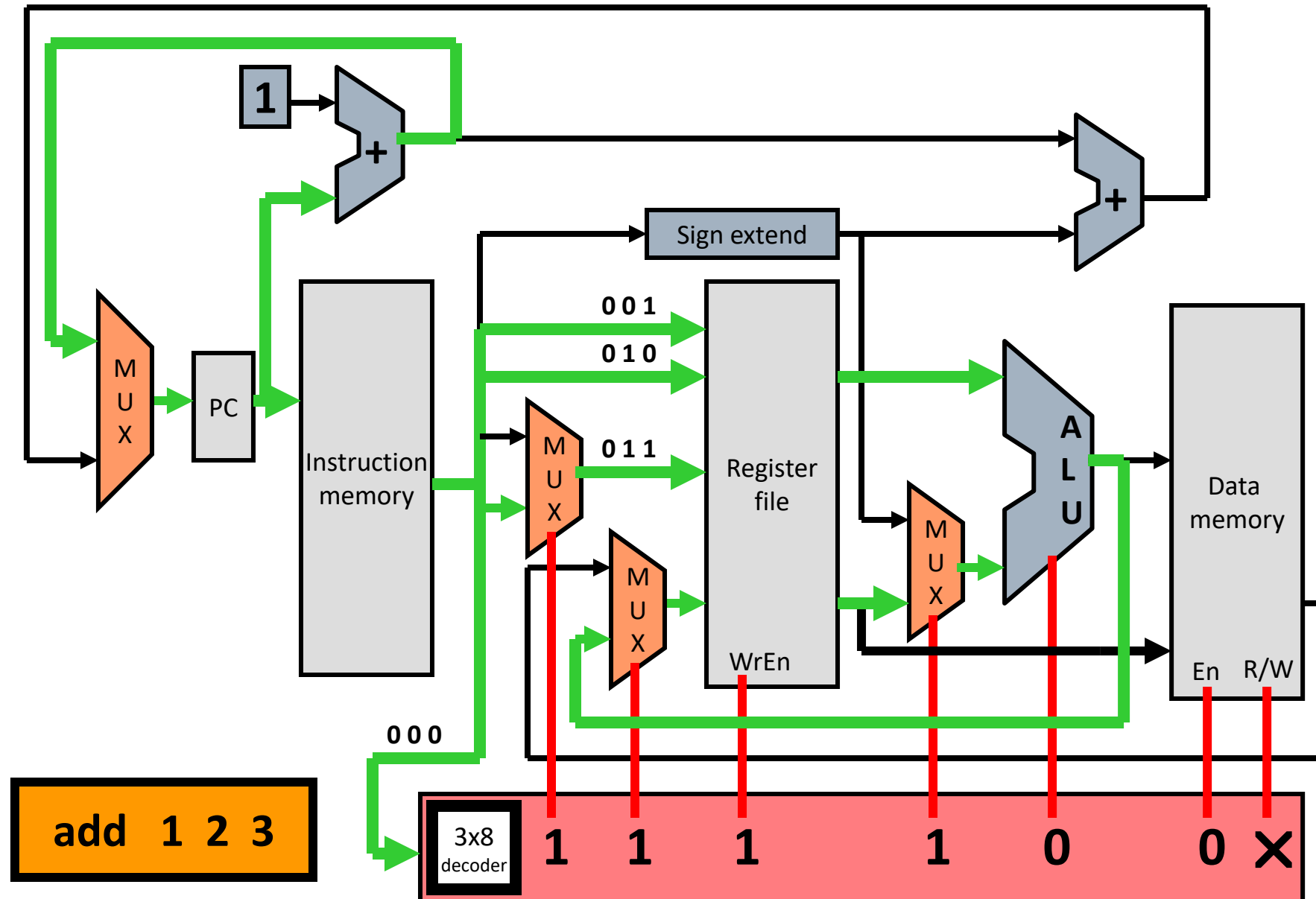Executing an **ADD** Instruction on LC2K Datapath




Poll: Which control bits need to be different from ADD?

Executing a **NOR** Instruction

 


Executing a **NOR** Instruction

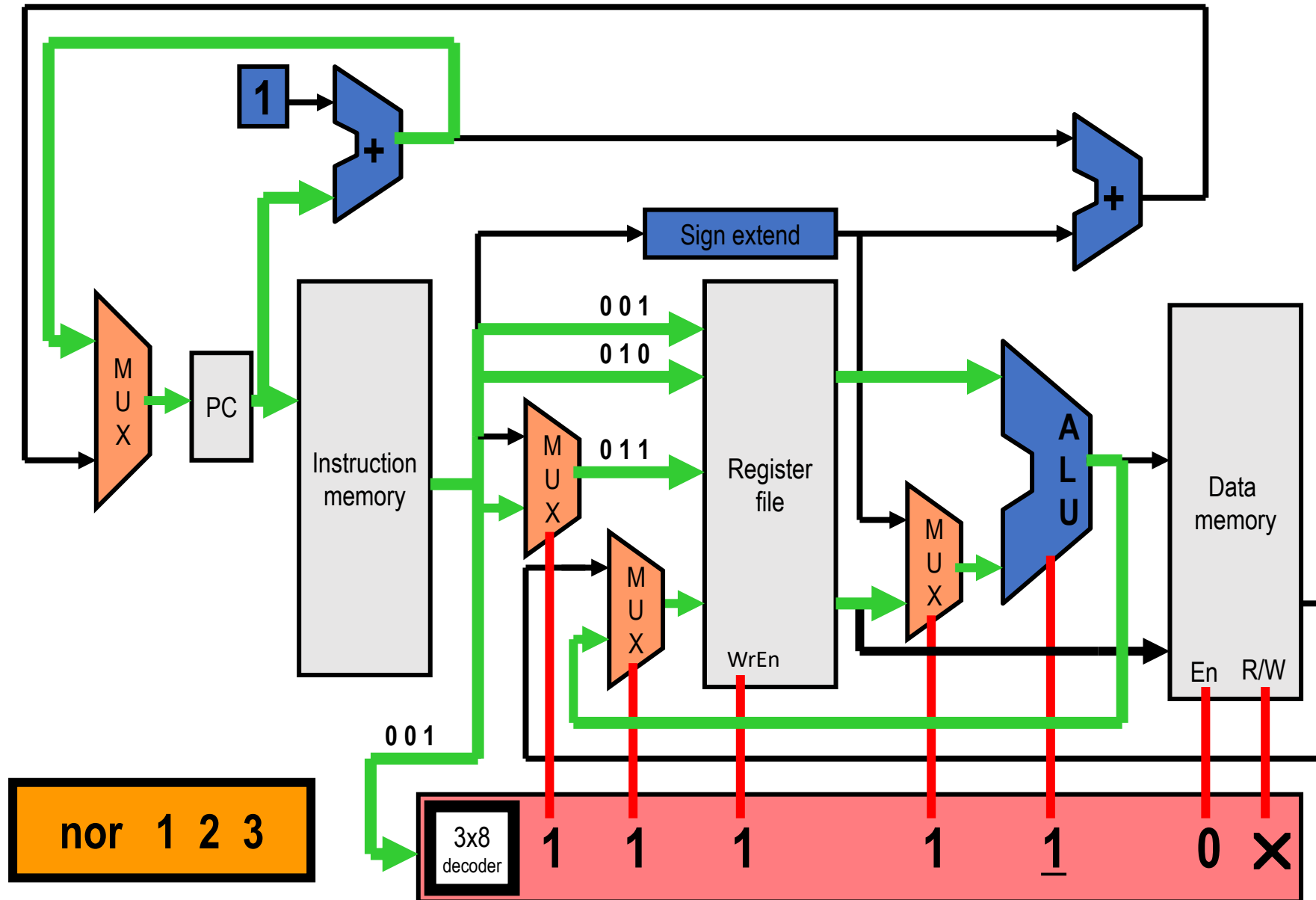


Executing a **LW** Instruction


31-25	24-22	21-19	18-16	15-0
unused	opcode	regA	regB	offset

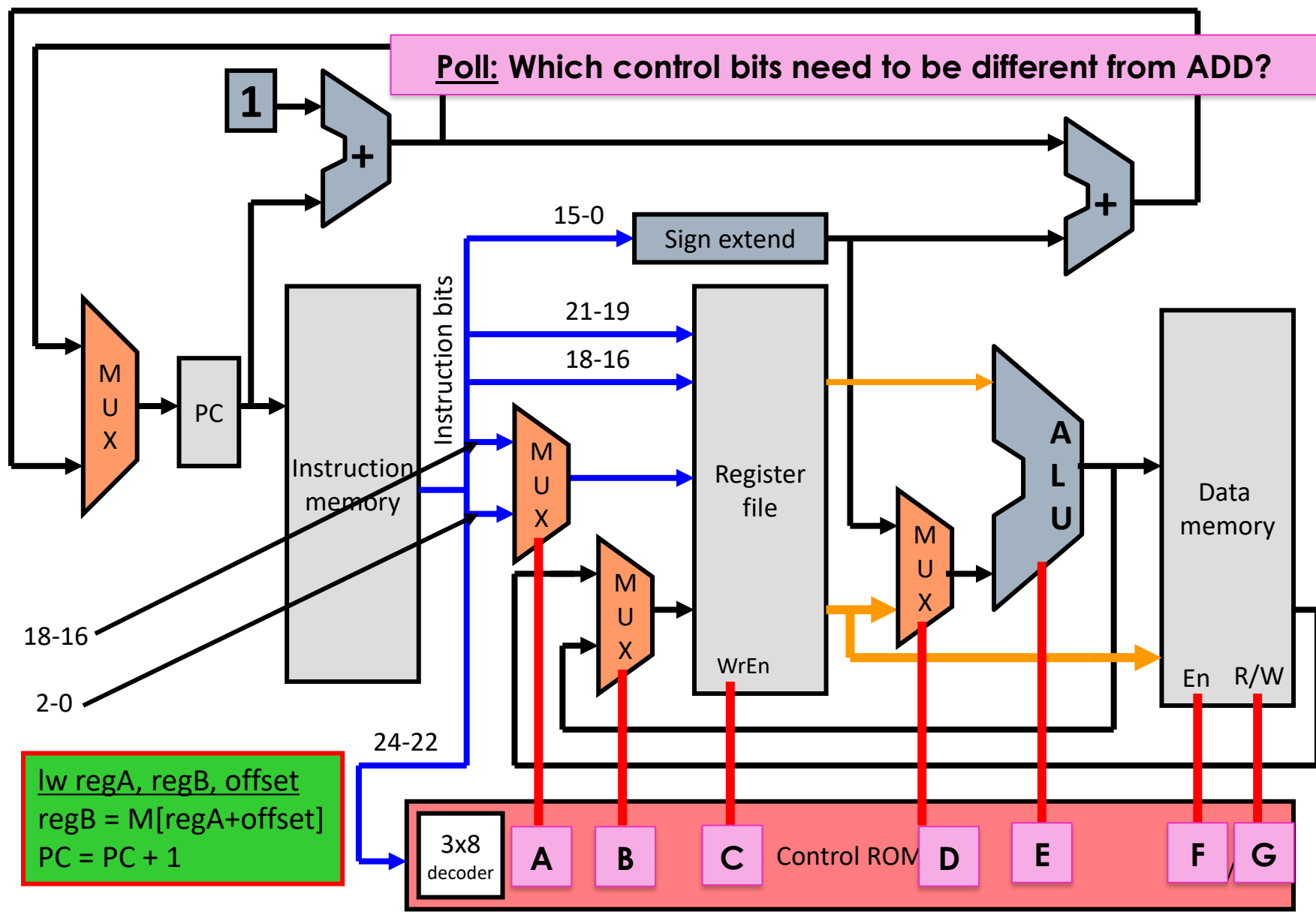


Executing a **LW** Instruction

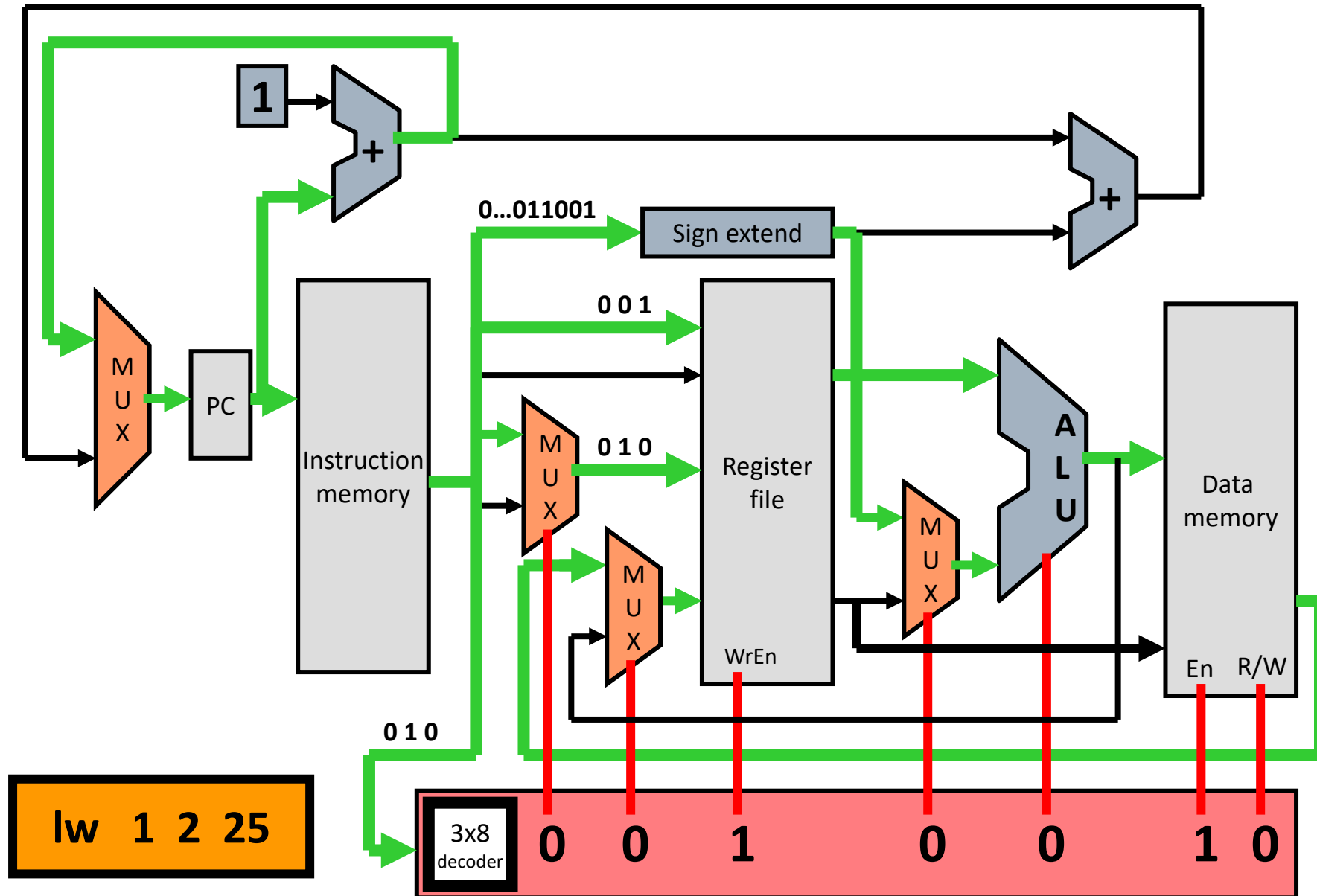


Executing a **SW** Instruction

 


Executing a **SW** Instruction

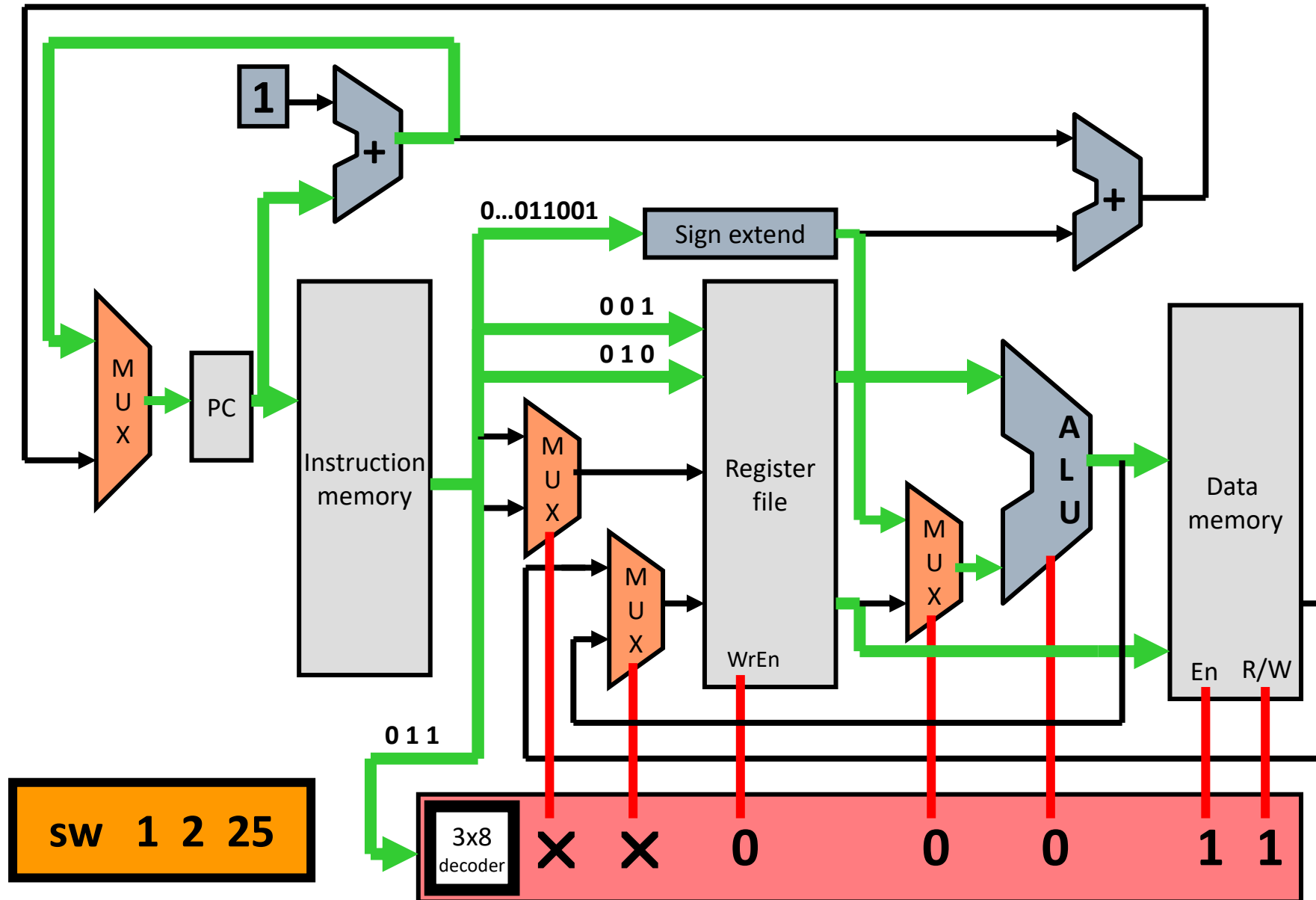


Executing a **BEQ** Instruction

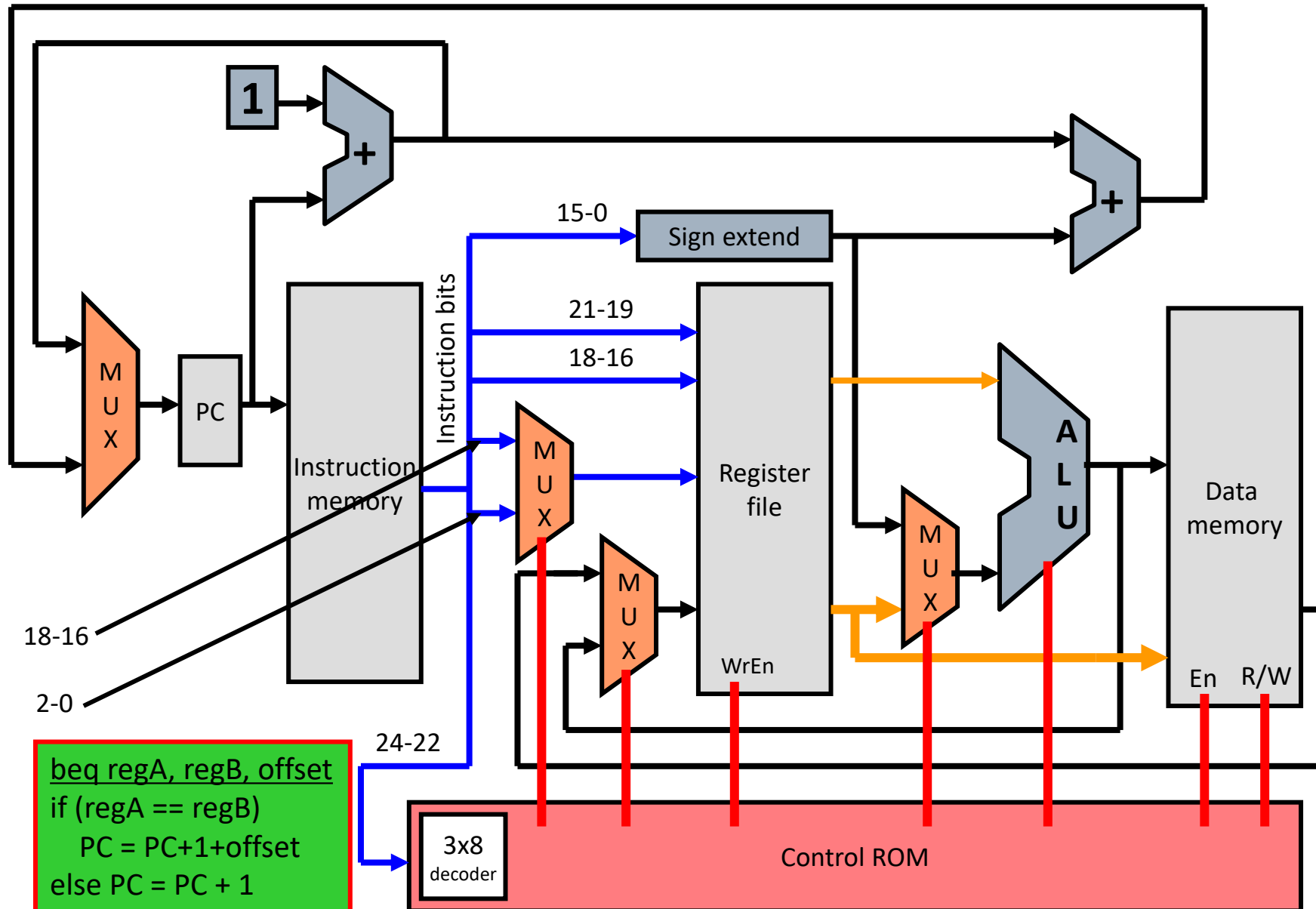

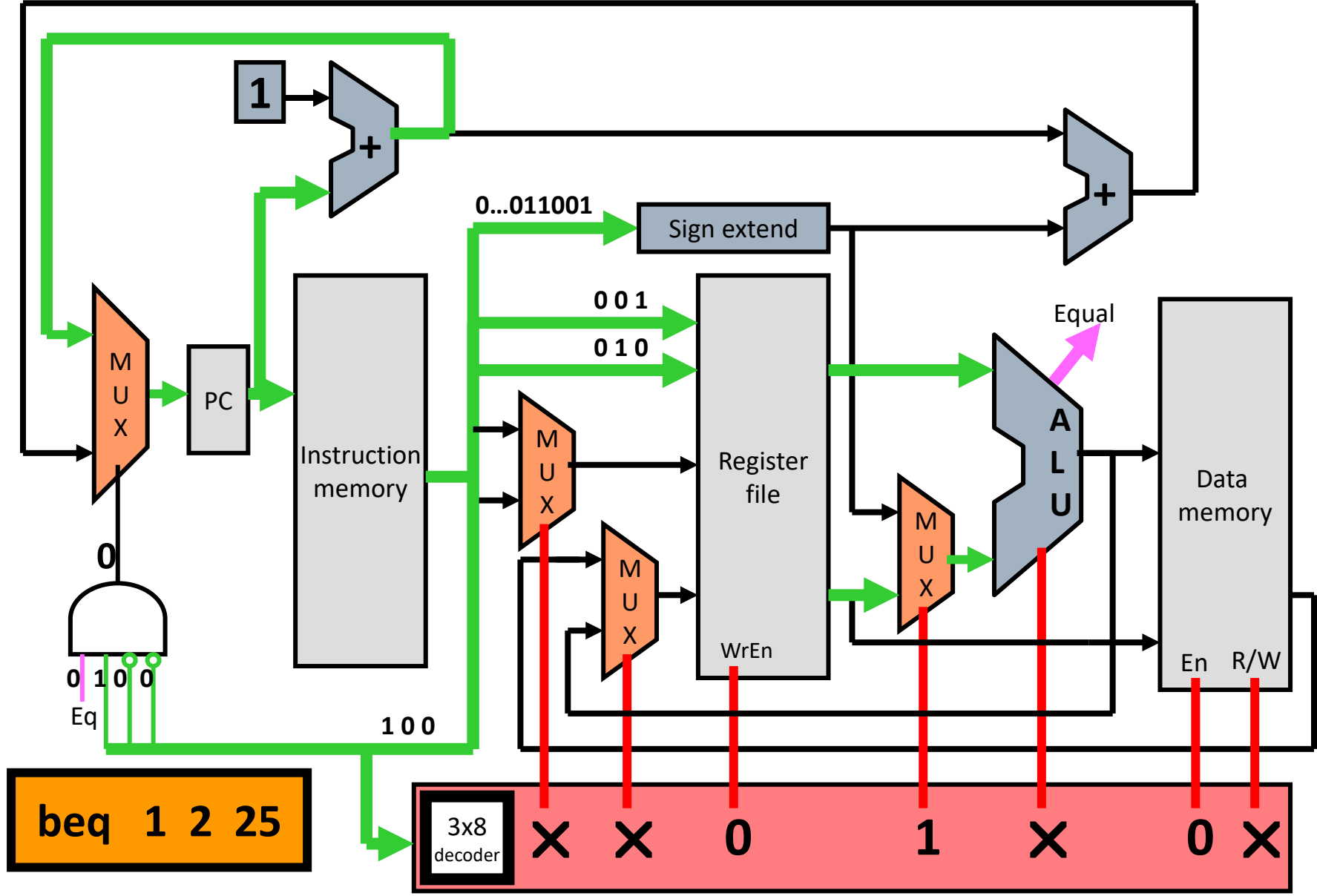Executing “not taken” **BEQ** Instruction on LC2K Datapath



 
Executing a “taken” **BEQ** Instruction on LC2K Datapath




So Far, So Good

- Every architecture seems to have at least one "ugly" instruction
 - Something that doesn't elegantly fit in with the hardware we've already included
- For LC2K, that ugly instruction is JALR
 - It doesn't fine into our nice clean datapath
- To implement JALR we need to:
 - Write $PC+1$ into regB
 - Move regA into PC
- Right now there is:
 - No path to write $PC+1$ into a register
 - No path to write a register to the PC


Executing a **JALR** Instruction

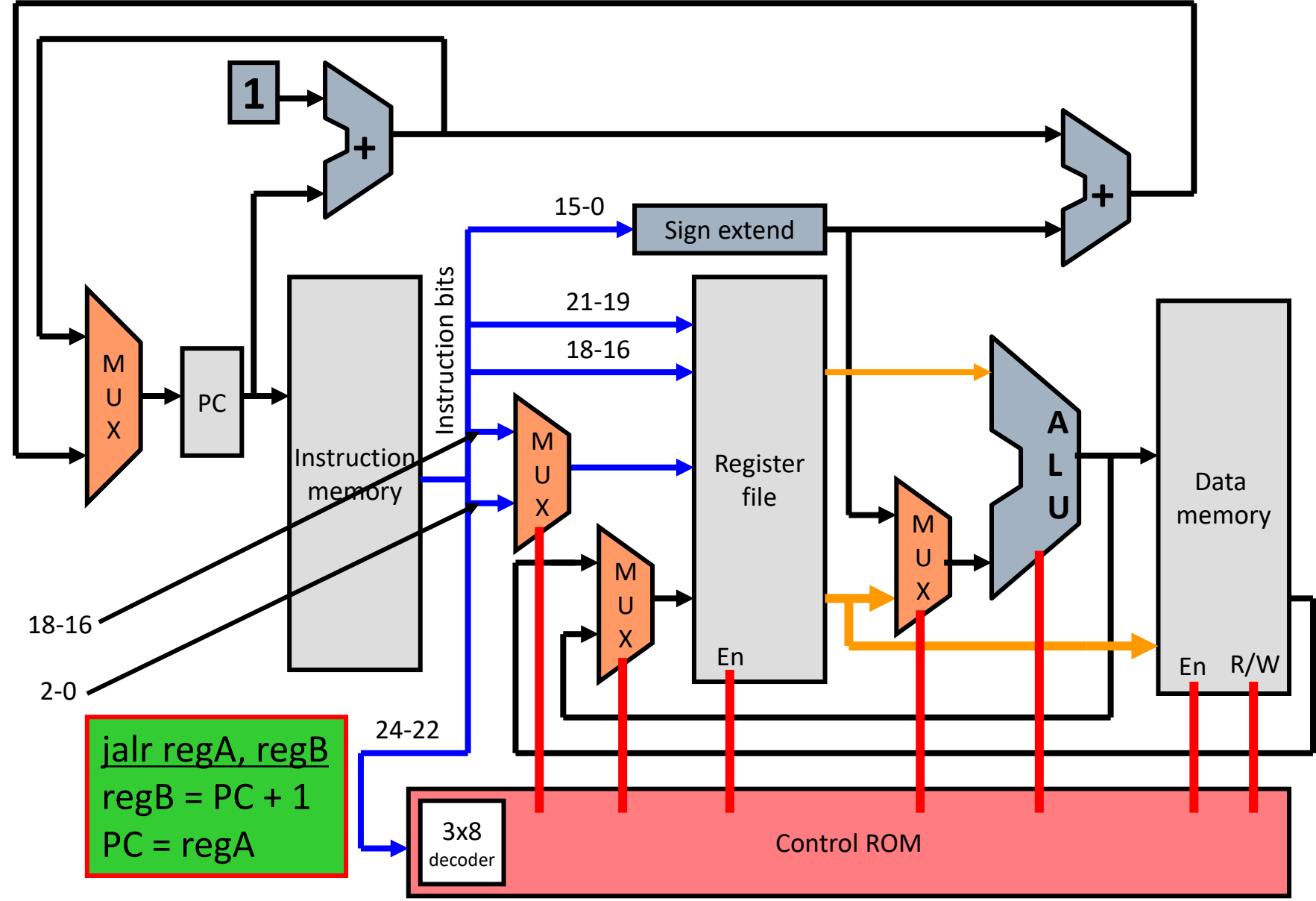


Executing a **JALR** Instruction

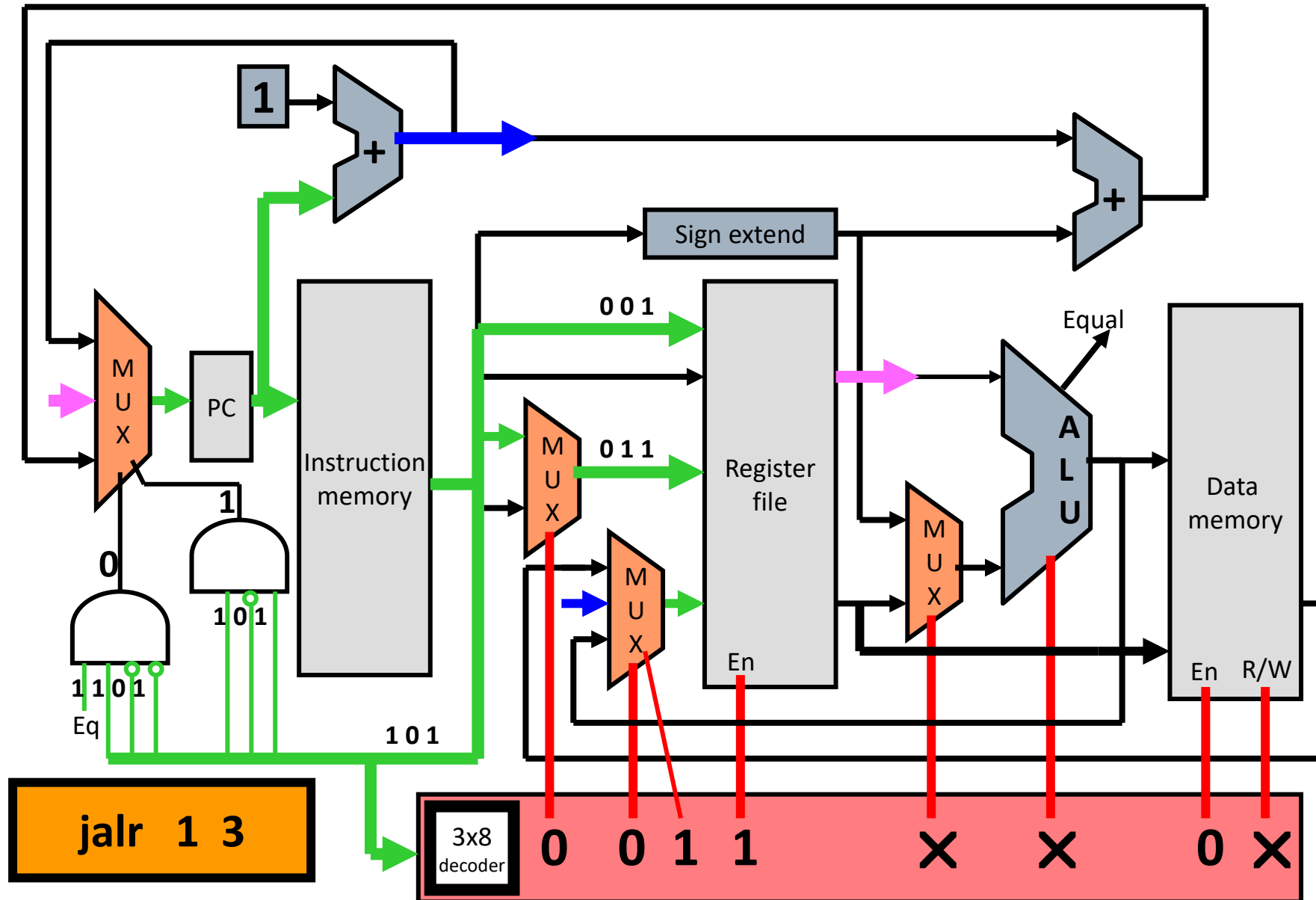

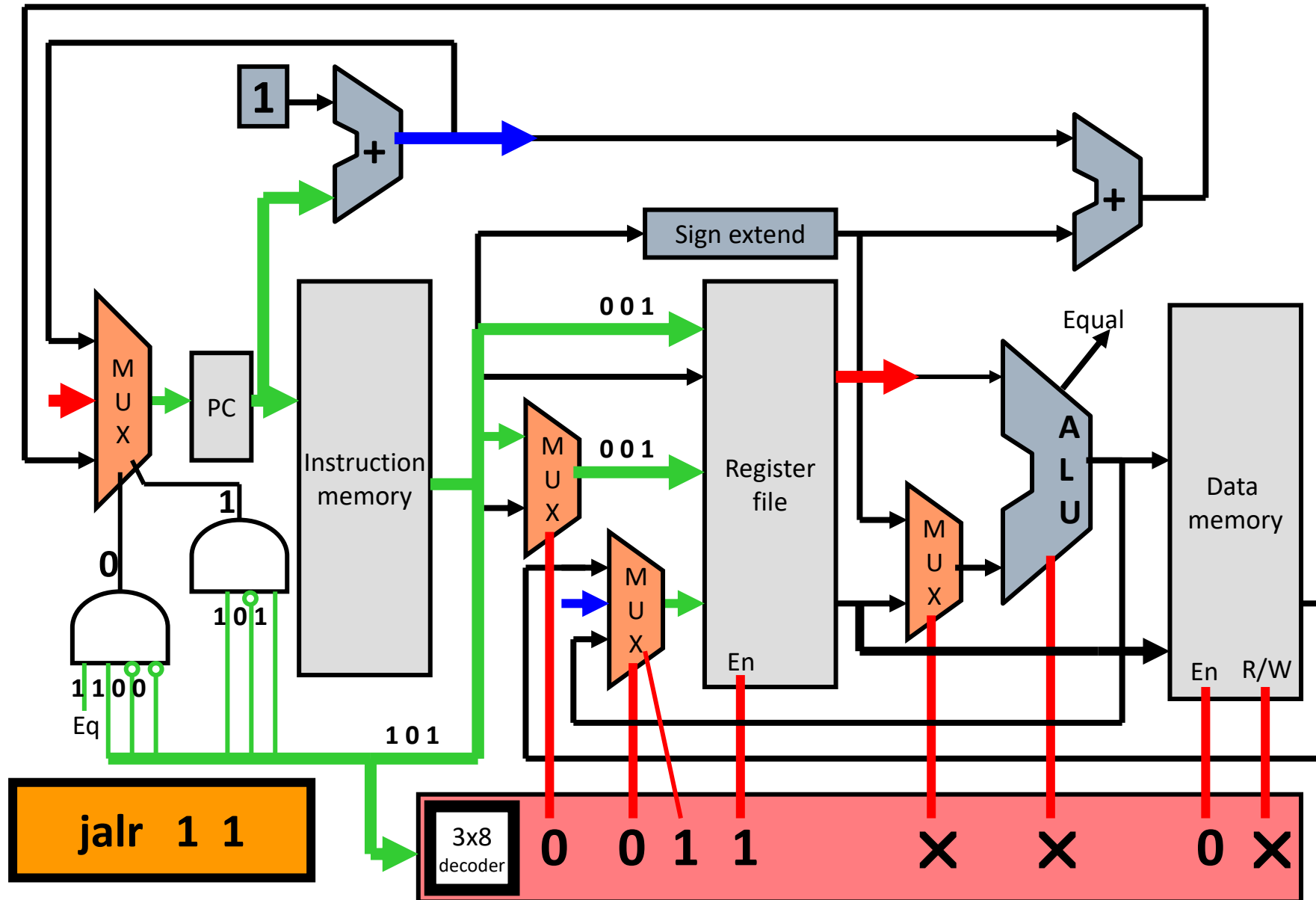What if $\text{regA} = \text{regB}$ for **JALR**?



Changes for **JALR 1 1** Instruction

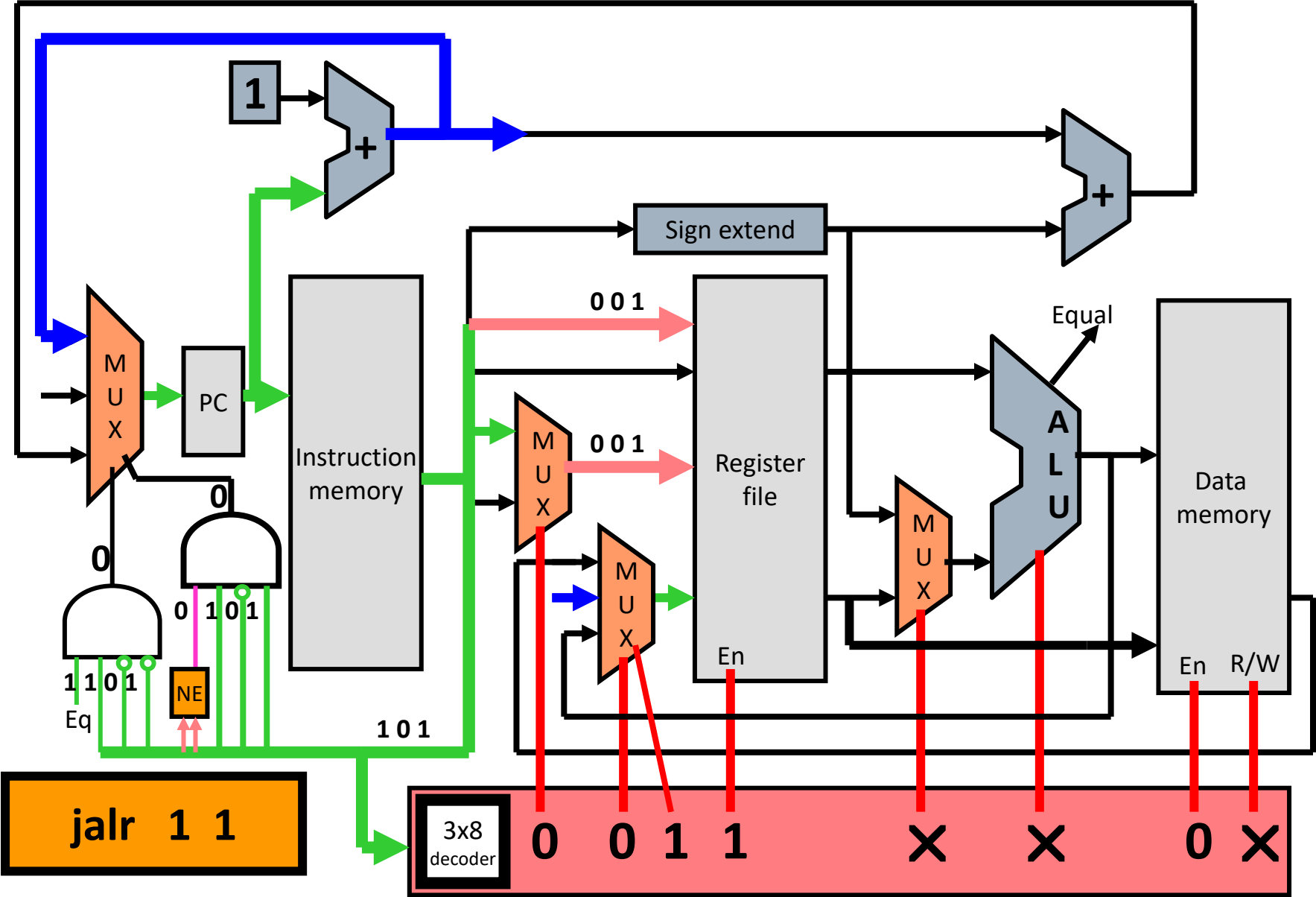

What's Wrong with Single-Cycle?

- **All instructions run at the speed of the slowest instruction.**
- Adding a long instruction can hurt performance
 - What if you wanted to include multiply?
- You cannot reuse any parts of the processor
 - We have 3 different adders to calculate $PC+1$, $PC+1+offset$ and the ALU
- No benefit in making the common case fast
 - Since every instruction runs at the slowest instruction speed
 - This is particularly important for loads as we will see later

What's Wrong with Single-Cycle?

- 1 ns – Register read/write time
- 2 ns – ALU/adder
- 2 ns – memory access
- 0 ns – MUX, PC access, sign extend, ROM

Poll: What is the latency of lw?

	Get Instr	read reg	ALU oper.	mem	write reg	
• add:	2ns	+ 1ns	+ 2ns		+ 1 ns	= 6 ns
• beq:	2ns	+ 1ns	+ 2ns			= 5 ns
• sw:	2ns	+ 1ns	+ 2ns	+ 2ns		= 7 ns
• lw:	2ns	+ 1ns	+ 2ns	+ 2ns	+ 1ns	= 8 ns

Computing Execution Time

Assume: 100 instructions executed

25% of instructions are loads,

10% of instructions are stores,

45% of instructions are adds, and

20% of instructions are branches.

Single-cycle execution:

??

Optimal execution:

??

Poll: What is the single-cycle execution time?

How fast could this run if we weren't limited by a single-clock period?

Computing Execution Time

Assume: 100 instructions executed

25% of instructions are loads,

10% of instructions are stores,

45% of instructions are adds, and

20% of instructions are branches.

Single-cycle execution:

$$100 * 8\text{ns} = \underline{\mathbf{800}} \text{ ns}$$


Optimal execution:

$$25*8\text{ns} + 10*7\text{ns} + 45*6\text{ns} + 20*5\text{ns} = \underline{\mathbf{640}} \text{ ns}$$


Multiple-Cycle Execution

- Each instruction takes multiple cycles to execute
 - Cycle time is reduced
 - Slower instructions take more cycles
 - Faster instructions take fewer cycles
 - We can start next instruction earlier, rather than just waiting
 - Can reuse datapath elements each cycle
- What is needed to make this work?
 - Since you are re-using elements for different purposes, you need more and/or wider MUXes.
 - You may need extra registers if you need to remember an output for 1 or more cycles.
 - Control is more complicated since you need to send new signals on each cycle.

LC2K Datapath – cycle groups

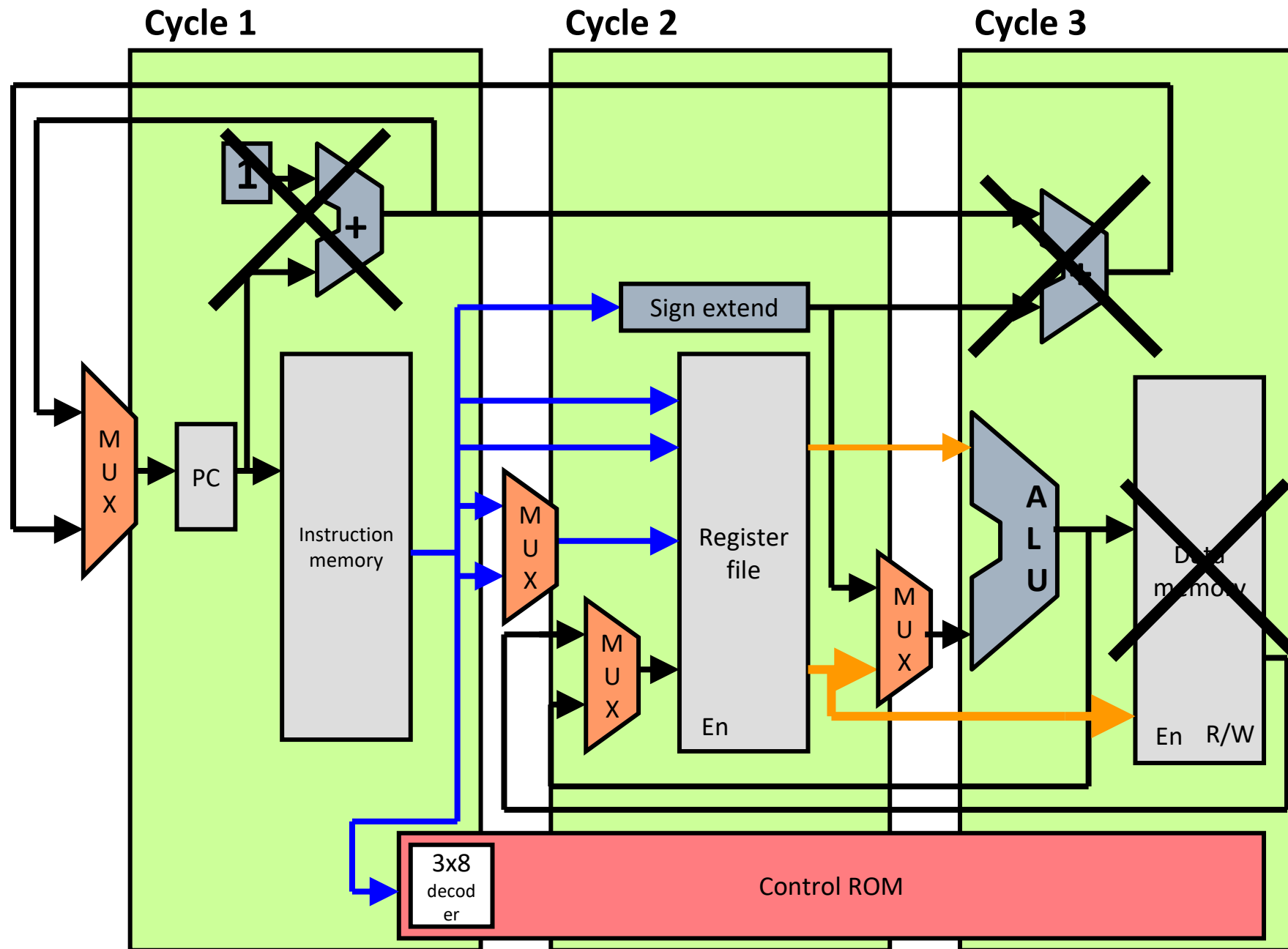


Multi-cycle LC2 Datapath

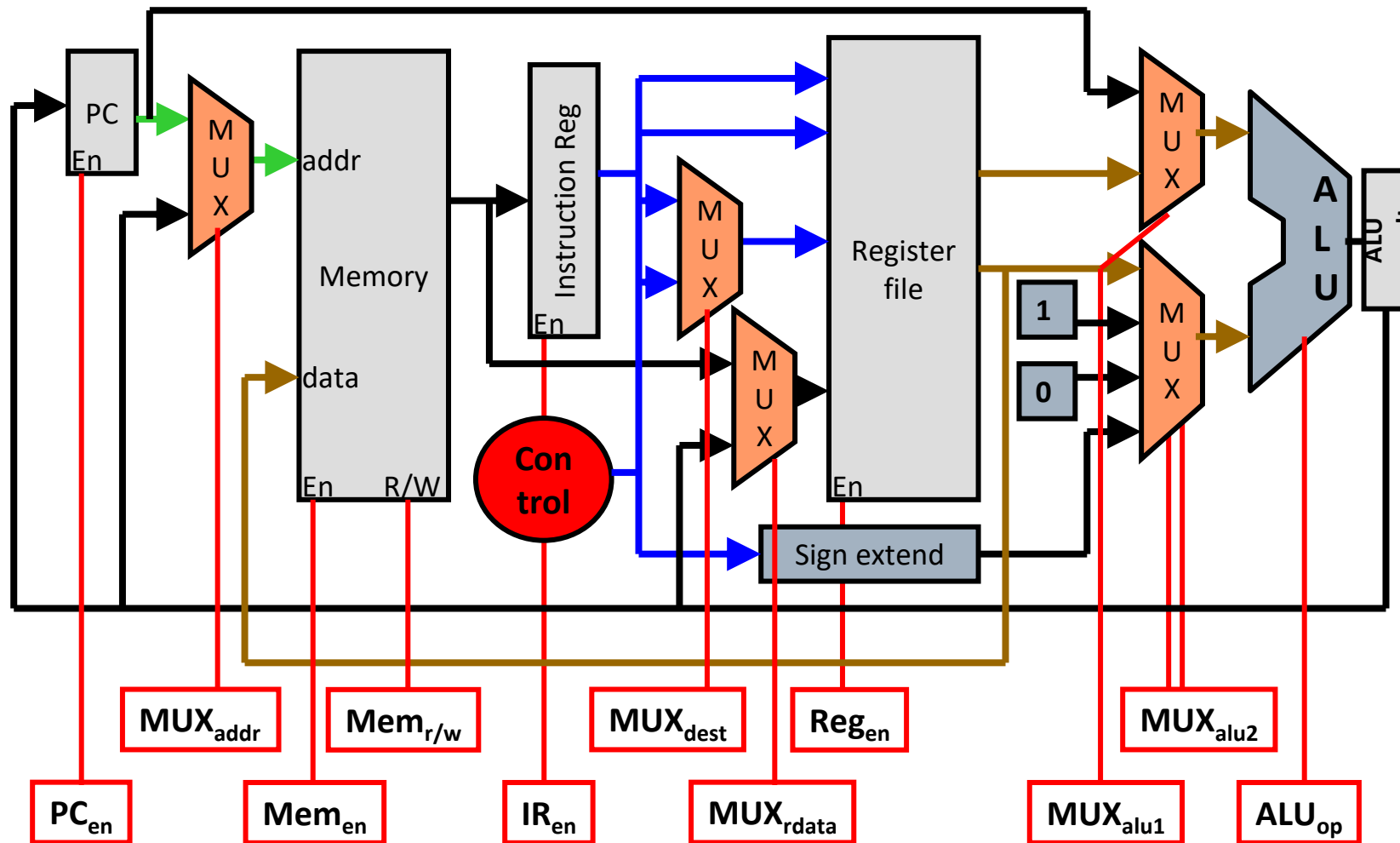

Each red signal comes from "Control"
(implemented via ROM as before)

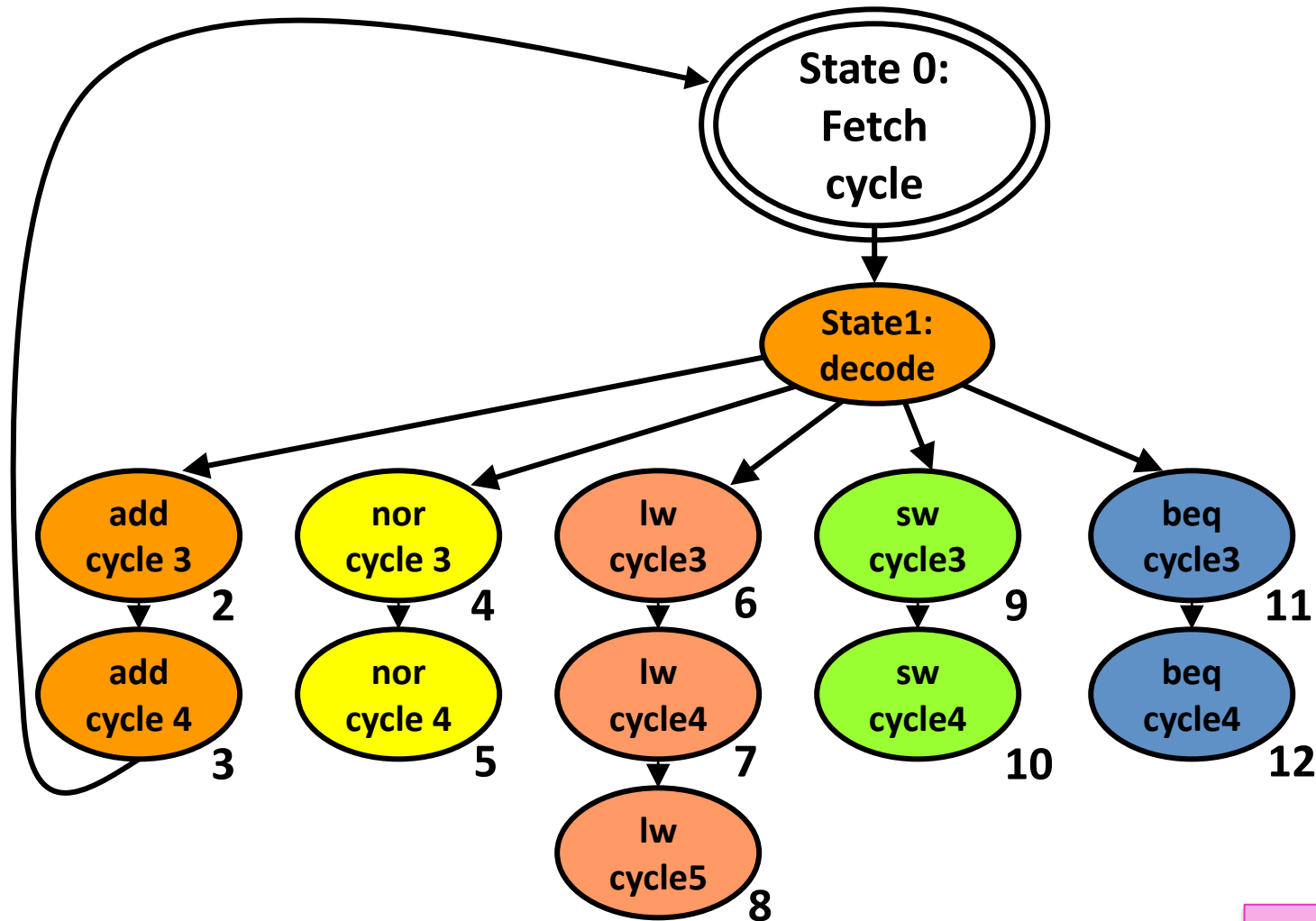
State machine for multi-cycle control signals (transition functions)




Note: we aren't worrying about JALR instruction in hardware going forward

Poll: How many bits of storage are needed to store the state?

Implementing FSM

 

Building the Control ROM

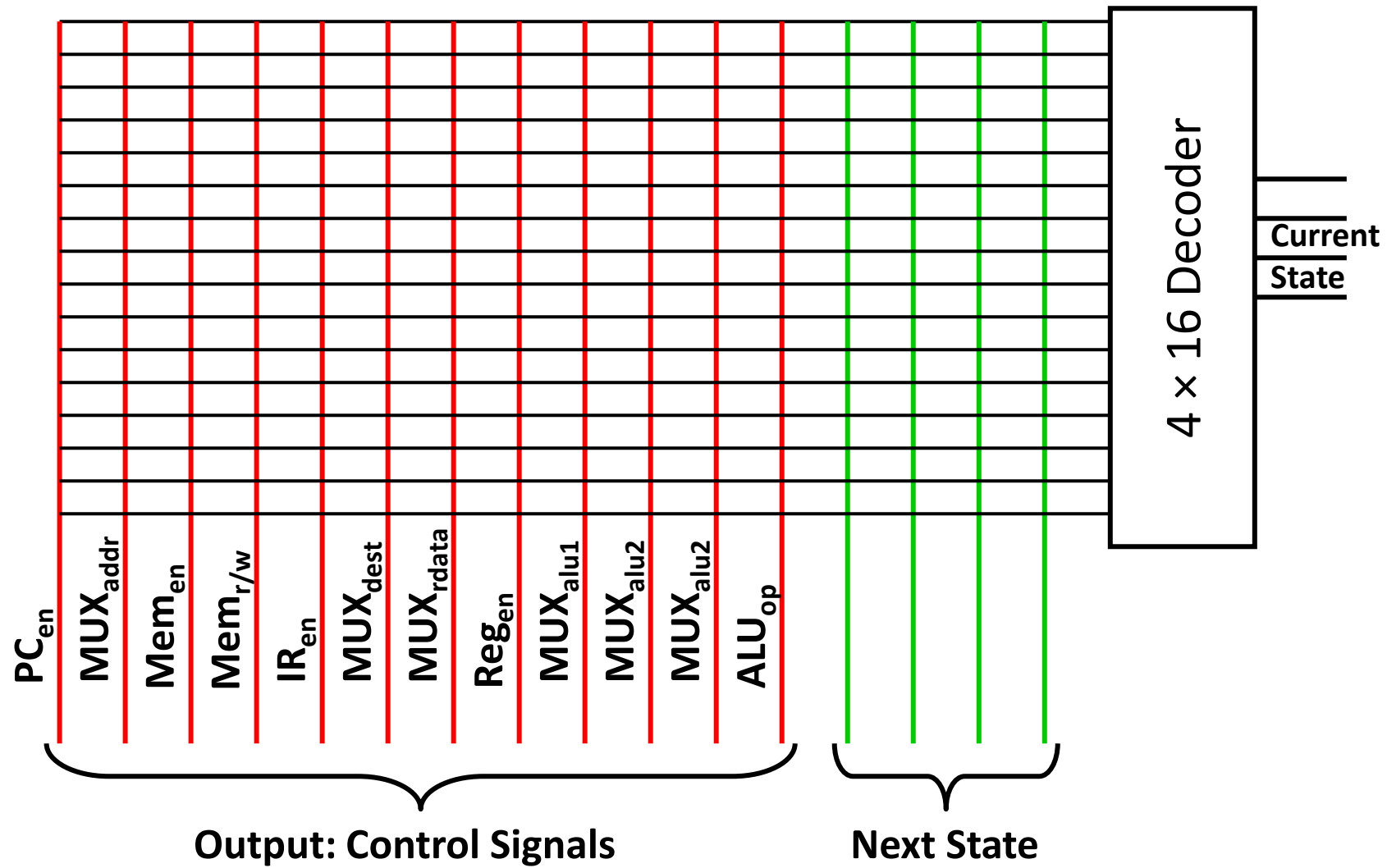


First Cycle (State 0) Fetch Instr

- What operations need to be done in the first cycle of executing any instruction?
 - Read memory[PC] and store into instruction register.
 - Must select PC in memory address MUX ($MUX_{addr} = 0$)
 - Enable memory operation ($Mem_{en} = 1$)
 - R/W should be (read) ($Mem_{r/w} = 0$)
 - Enable Instruction Register write ($IR_{en} = 1$)
 - Calculate PC + 1
 - Send PC to ALU ($MUX_{alu1} = 0$)
 - Send 1 to ALU ($MUX_{alu2} = 01$)
 - Select ALU add operation ($ALU_{op} = 0$)
 - $PC_{en} = 0$; $Reg_{en} = 0$; MUX_{dest} and $MUX_{rdata} = X$
- Next State: Decode Instruction


First Cycle (State 0) Fetch Instr

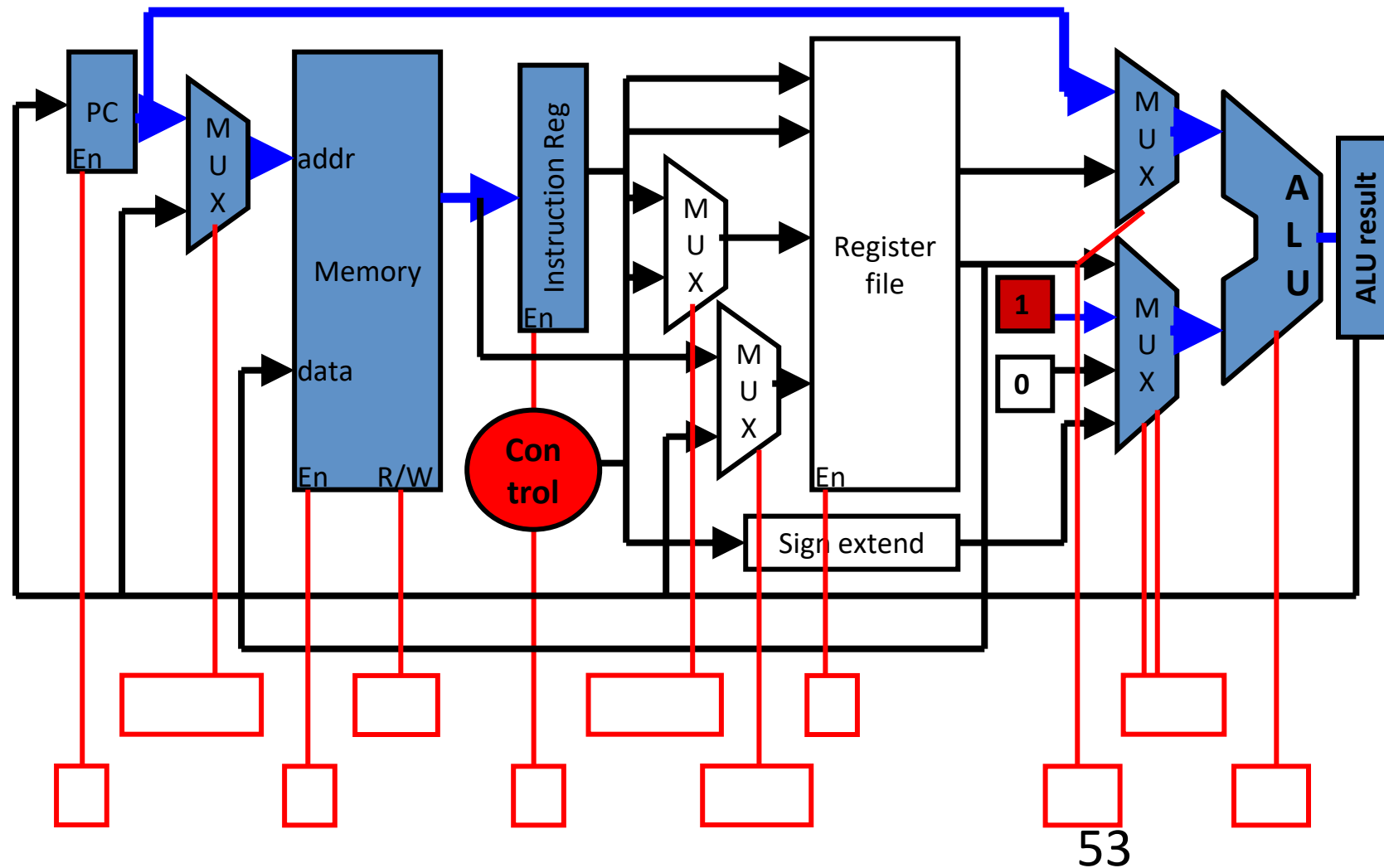This is the same for all instructions
(since we don't know the instruction yet!)




First Cycle (State 0) Fetch Instr

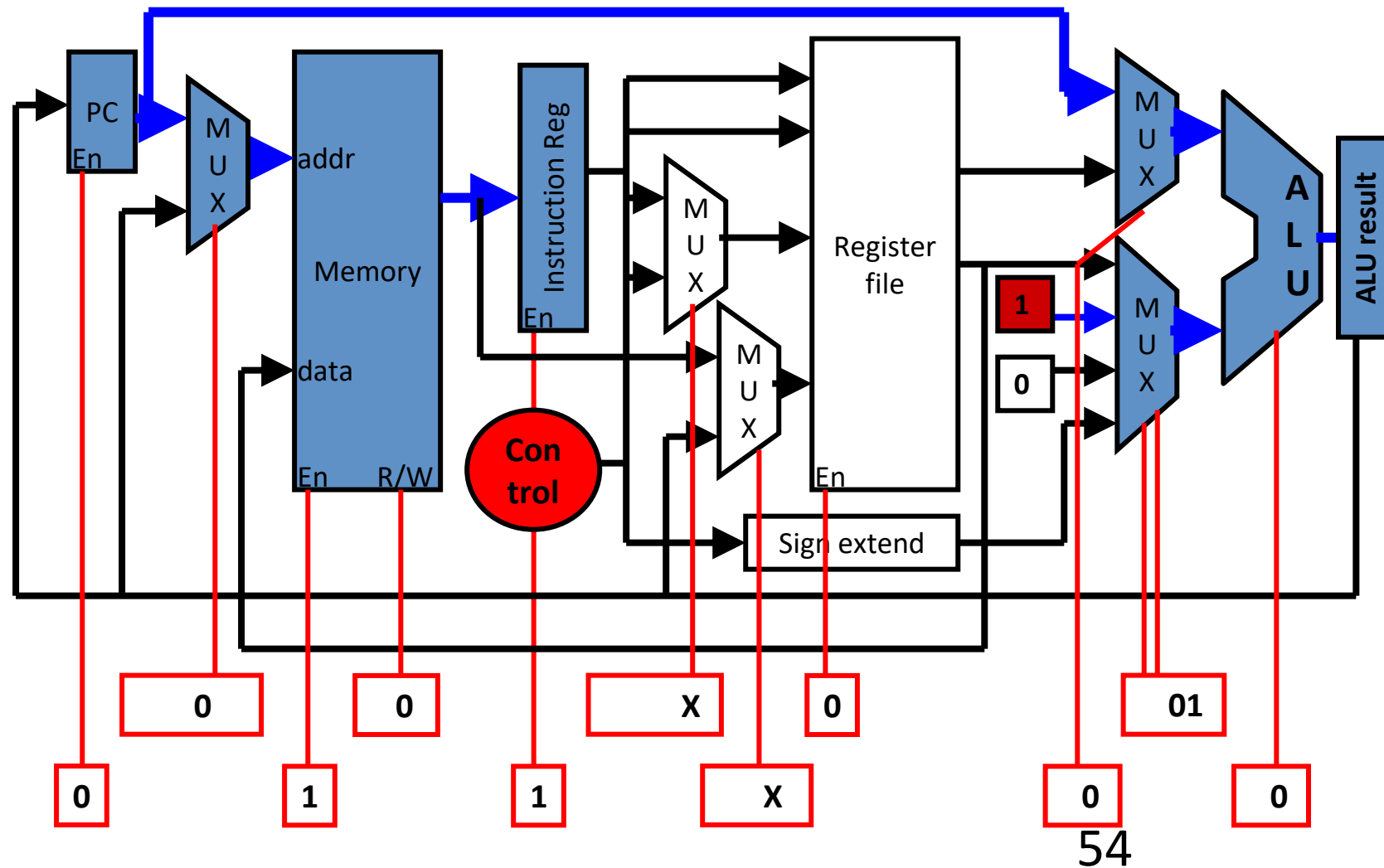This is the same for all instructions
(since we don't know the instruction yet!)



Building the Control ROM

 

Next time

- Finish up multi-cycle processors
- Introduce pipelining