

EECS 370 - Lecture 12

Multi-cycle + Introduction to Pipelining



Reminder

- If you're watching lectures asynchronously...
- I have studio recordings
 - Much better quality than lecture recordings
 - I won't walk off screen, etc



Announcements

- P2
 - Three parts: part a is due **Thursday**
- HW 2
 - Posted on website, due next **Mon**
- Lab due Wed @ 11:55 pm
 - Lab meets Fr/M before exam, not after exam
- Midterm exam **Wed 7-9 pm**
 - Sample exams on website
 - You can bring 1 sheet (double sided is fine) of notes
 - We will provide LC2K encodings + ARM cheat sheet
 - Calculator that doesn't connect to internet is recommended

Midterm Review

- Staff led review session on Sunday
 - Will be recorded, see Ed post
- Lecture on Tuesday will also be review

What's Wrong with Single-Cycle?

- 1 ns – Register read/write time
- 2 ns – ALU/adder
- 2 ns – memory access
- 0 ns – MUX, PC access, sign extend, ROM

	Get Instr	read reg	ALU oper.	mem	write reg	
• add:	2ns	+ 1ns	+ 2ns		+ 1 ns	= 6 ns
• beq:	2ns	+ 1ns	+ 2ns			= 5 ns
• sw:	2ns	+ 1ns	+ 2ns	+ 2ns		= 7 ns
• lw:	2ns	+ 1ns	+ 2ns	+ 2ns	+ 1ns	= 8 ns


Review: What's Wrong with Single-Cycle?

- **All instructions run at the speed of the slowest instruction.**
- Adding a long instruction can hurt performance
 - What if you wanted to include multiply?
- You cannot reuse any parts of the processor
 - We have 3 different adders to calculate $PC+1$, $PC+1+offset$ and the ALU
- No benefit in making the common case fast
 - Since every instruction runs at the slowest instruction speed
 - This is particularly important for loads as we will see later

Multiple-Cycle Execution


- Each instruction takes multiple cycles to execute
 - Cycle time is reduced
 - Slower instructions take more cycles
 - Faster instructions take fewer cycles
 - We can start next instruction earlier, rather than just waiting
 - Can reuse datapath elements each cycle
- What is needed to make this work?
 - Since you are re-using elements for different purposes, you need more and/or wider MUXes.
 - You may need extra registers if you need to remember an output for 1 or more cycles.
 - Control is more complicated since you need to send new signals on each cycle.

Multi-cycle LC2 Datapath

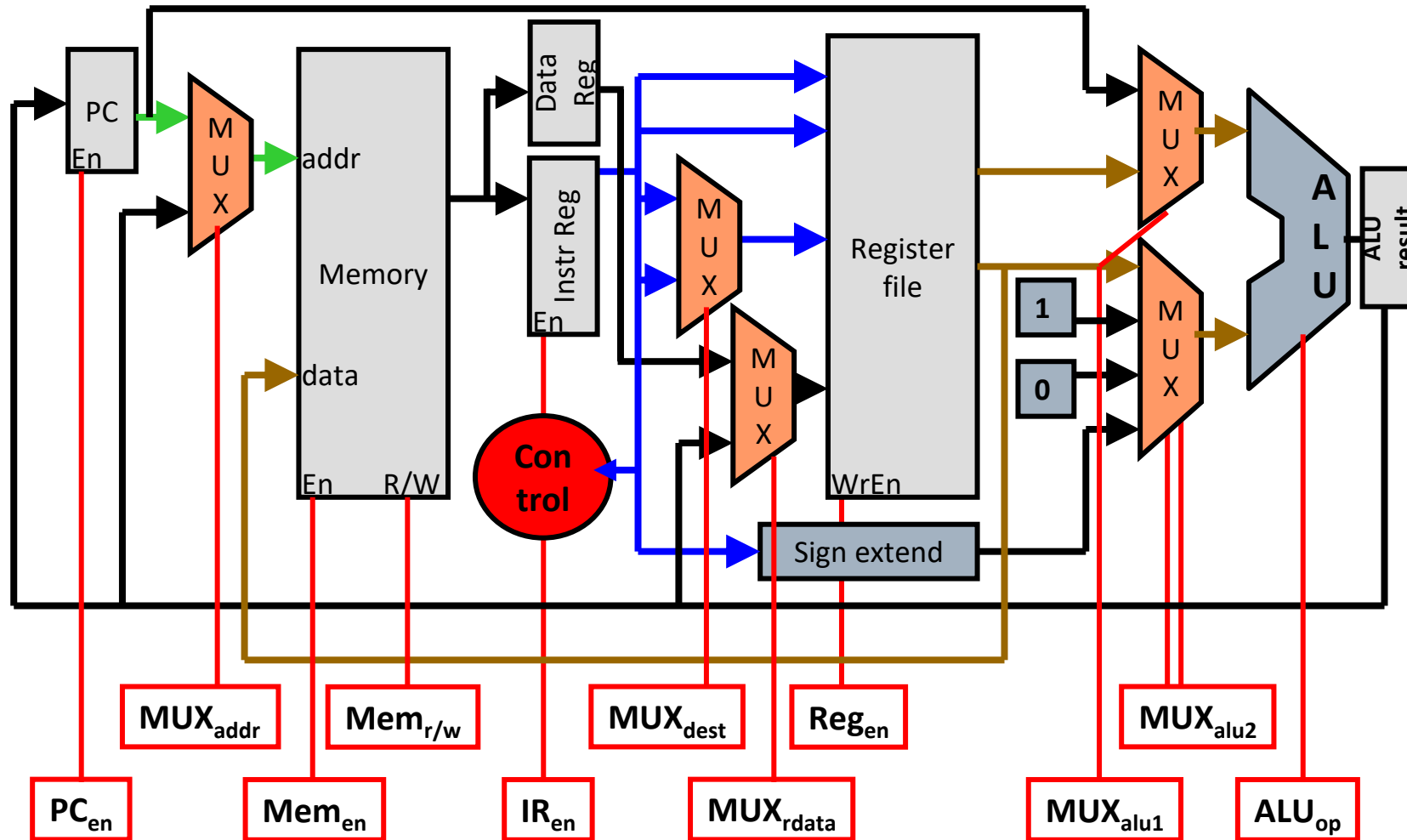


Each red signal comes from "Control"
(implemented via ROM as before)

 State machine for multi-cycle control signals (transition functions)




Note: we aren't worrying about JALR instruction in hardware going forward

Implementing FSM

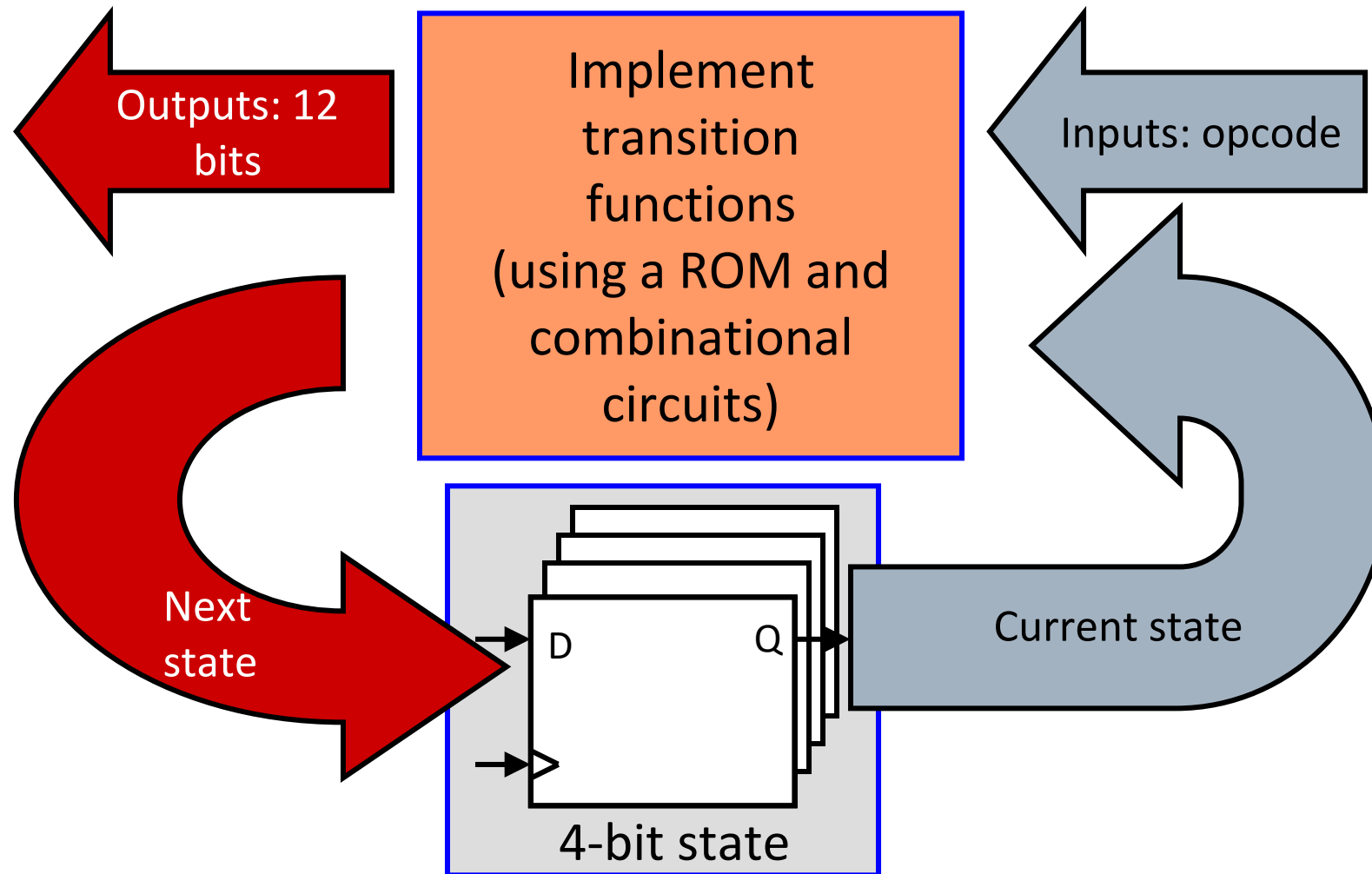

Building the Control ROM

 


First Cycle (State 0) Fetch Instr


- What operations need to be done in the first cycle of executing any instruction?
 - Read memory[PC] and store into instruction register.
 - Must select PC in memory address MUX ($MUX_{addr} = 0$)
 - Enable memory operation ($Mem_{en} = 1$)
 - R/W should be (read) ($Mem_{r/w} = 0$)
 - Enable Instruction Register write ($IR_{en} = 1$)
 - Calculate PC + 1
 - Send PC to ALU ($MUX_{alu1} = 0$)
 - Send 1 to ALU ($MUX_{alu2} = 01$)
 - Select ALU add operation ($ALU_{op} = 0$)
 - $PC_{en} = 0$; $Reg_{en} = 0$; MUX_{dest} and $MUX_{rdata} = X$
- Next State: Decode Instruction

First Cycle (State 0) Fetch Instr

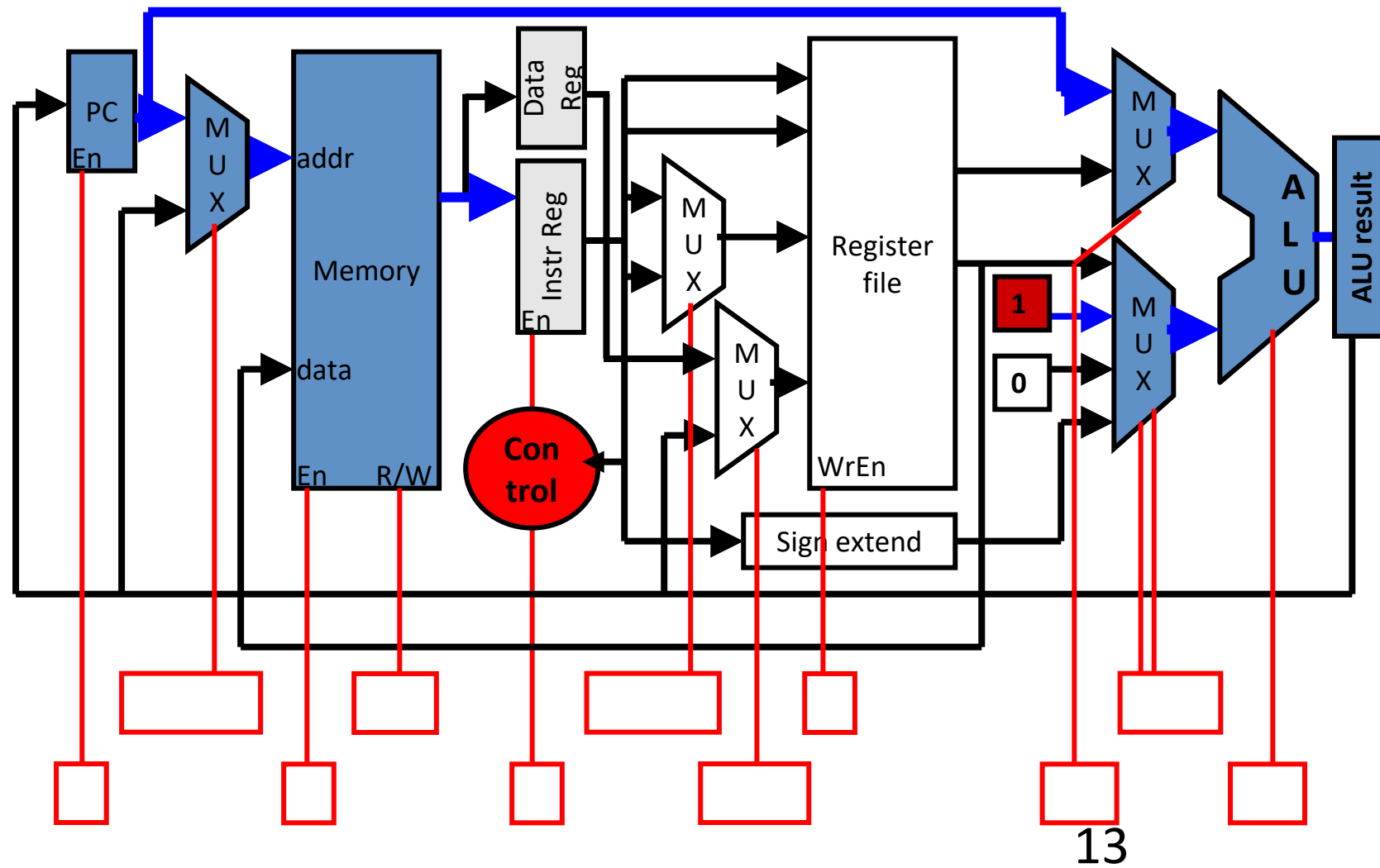
This is the same for all instructions
(since we don't know the instruction yet!)



Building the Control ROM

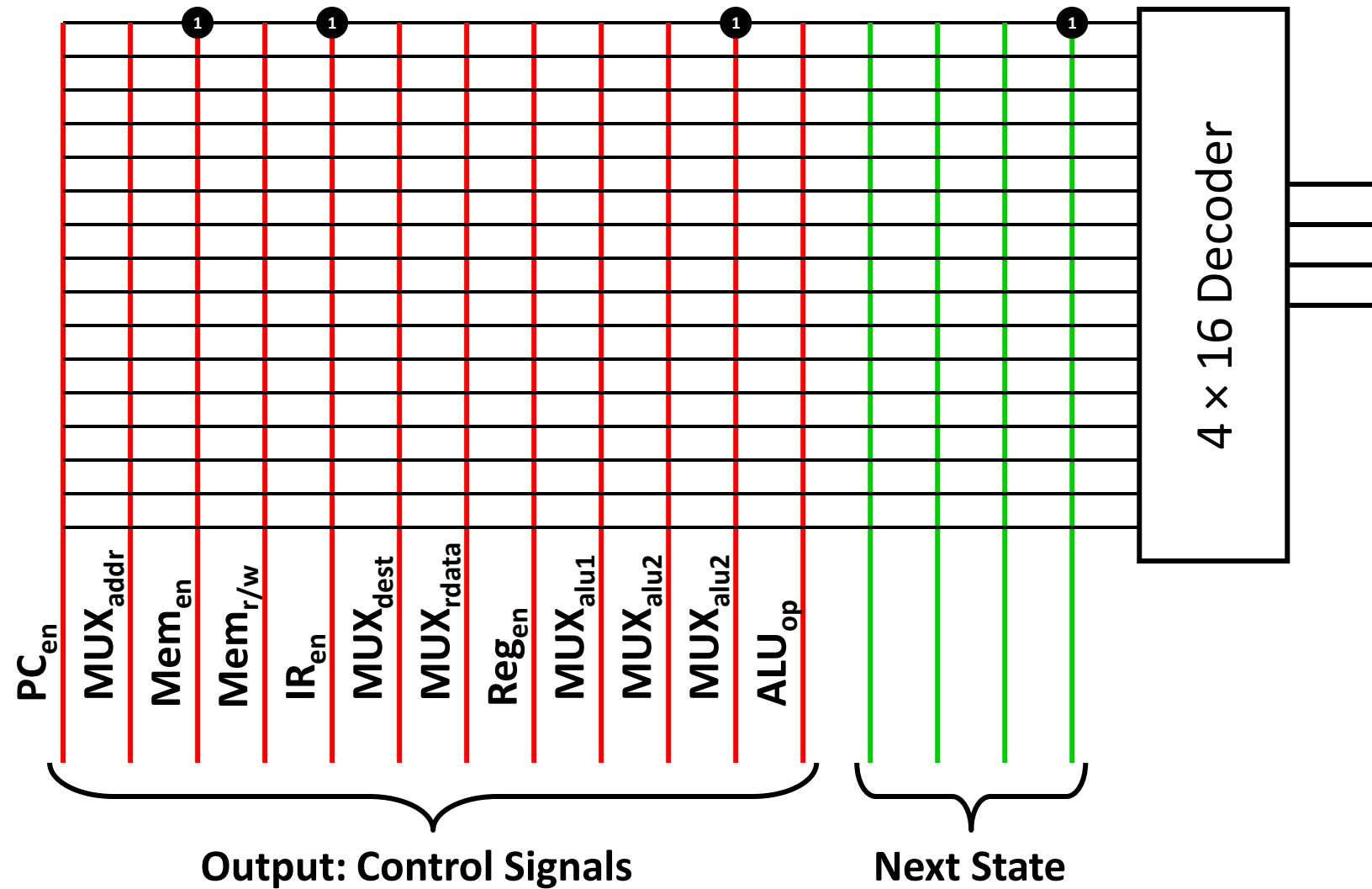

State 1: instruction decode

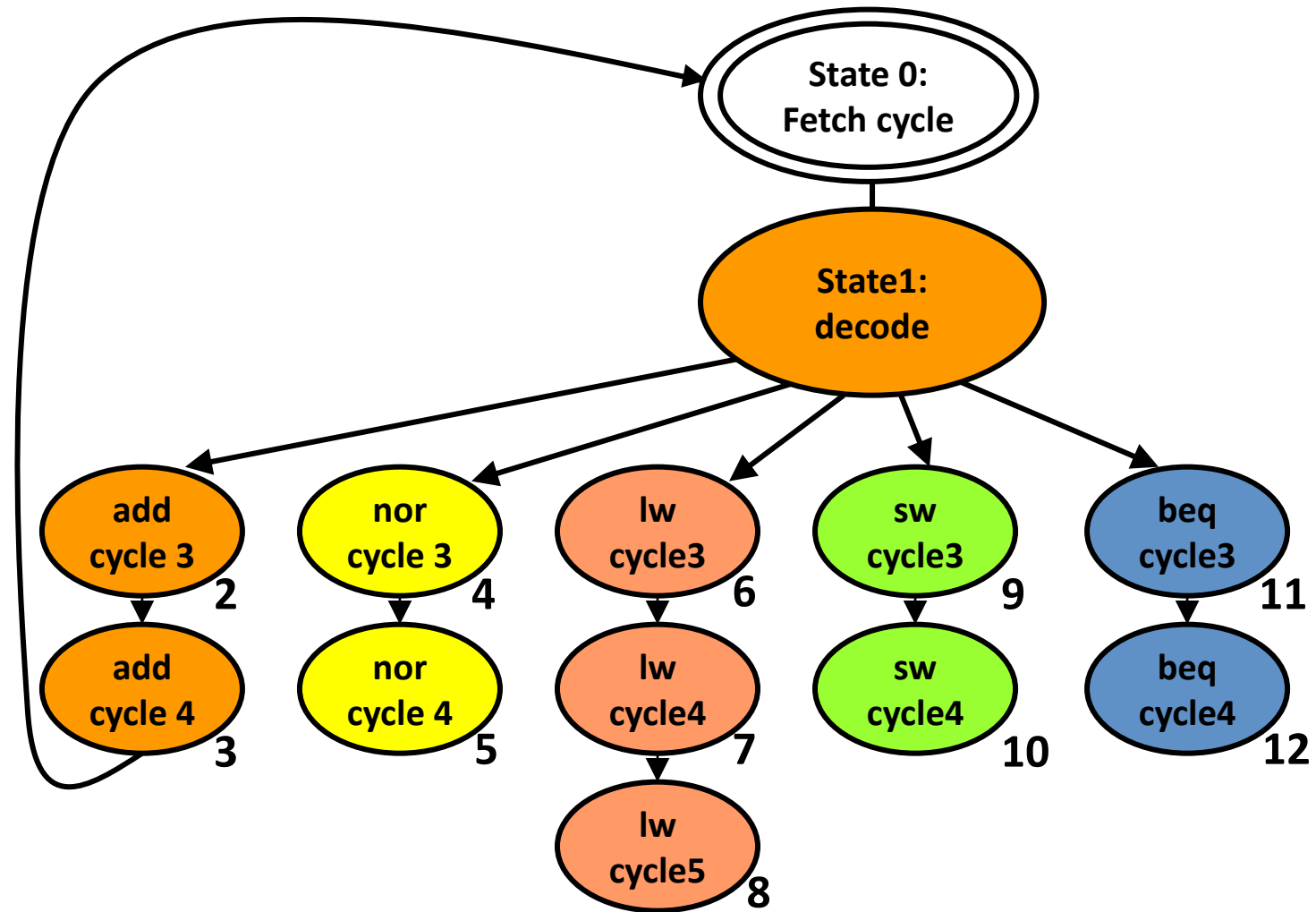


State 1: output function

Poll: What will the control bits be?


Update PC; read registers (regA and regB);
use opcode to determine next state

Note: since RF read
latency is same as
clock period, RF
data isn't available
until next cycle

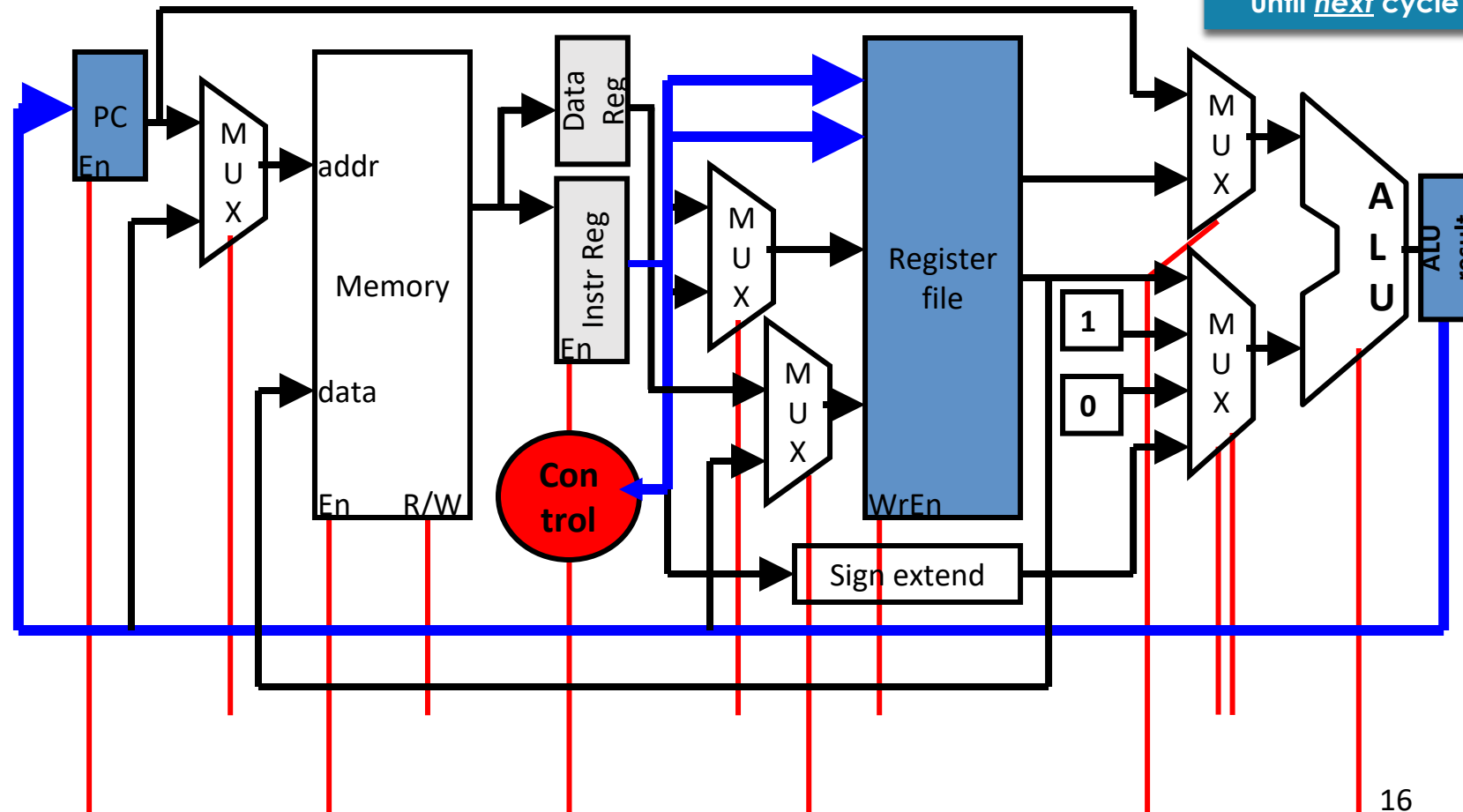

State 1: output function

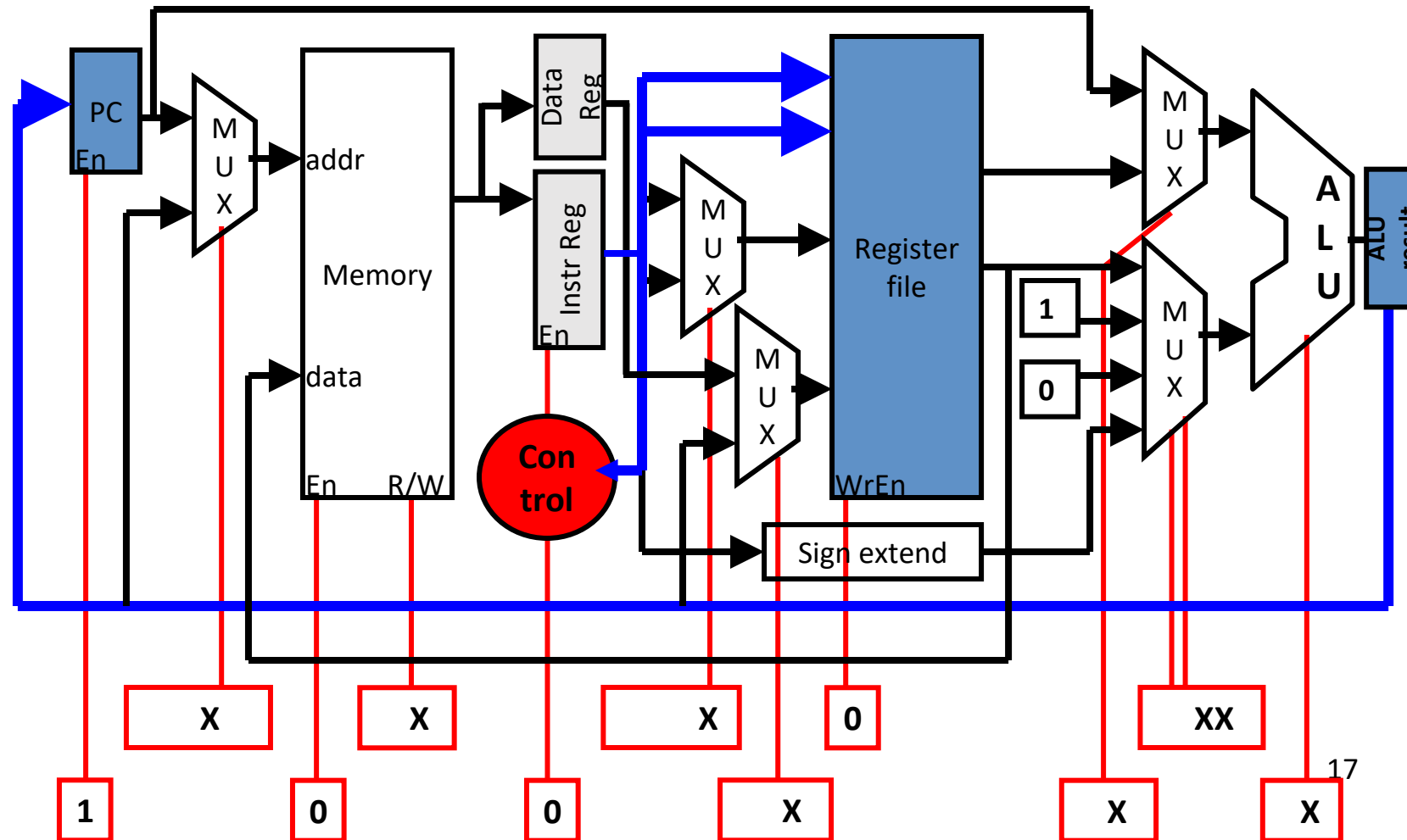
Update PC; read registers (regA and regB);
use opcode to determine next state



Transitioning from Decode State

Which state we go to depends on opcode, can't just look at current state like before

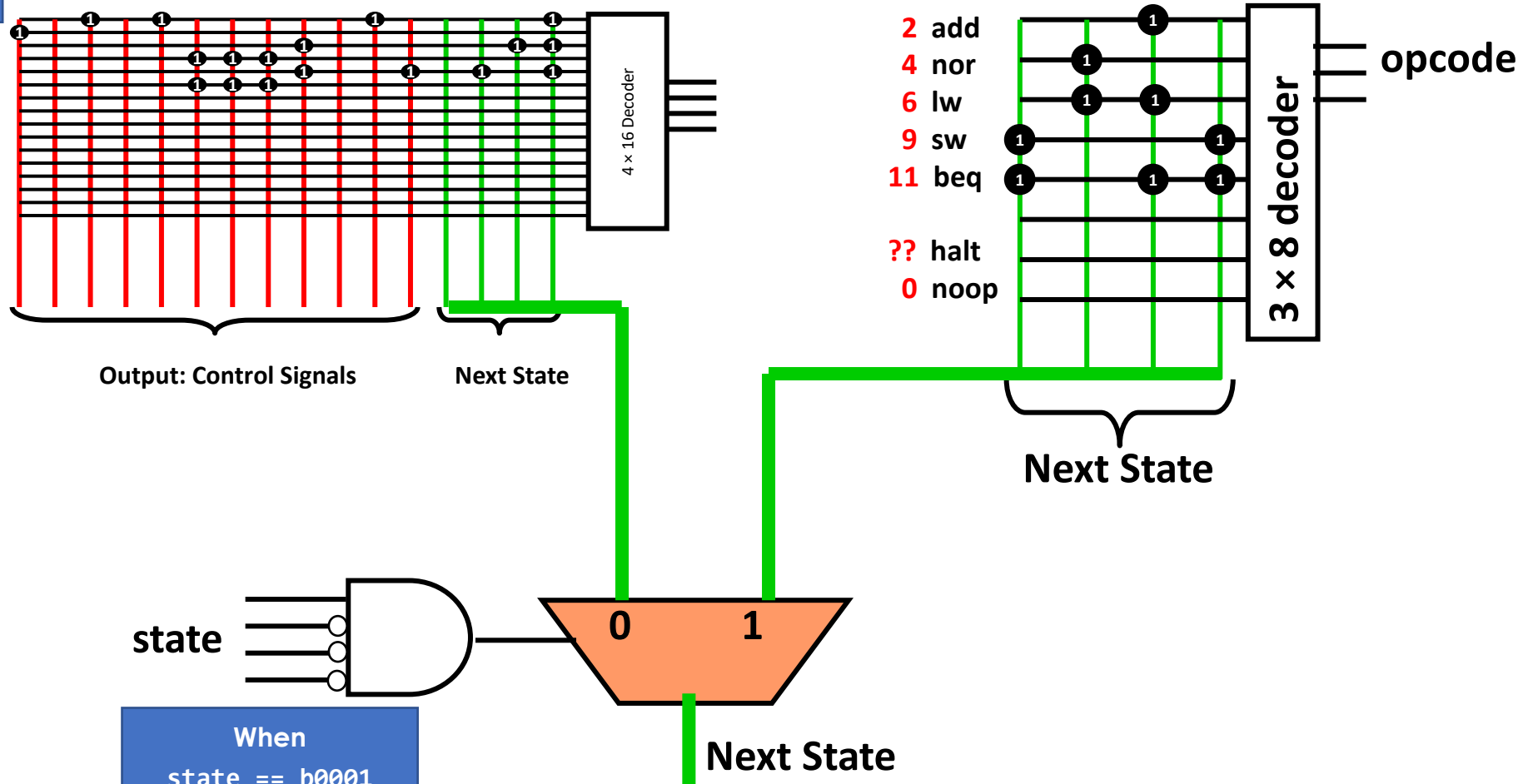
Secondary ROM stores which state we should branch to after decode for each opcode



When
state == b0001
choose secondary
ROM for next state
logic




State 2: Add cycle 3

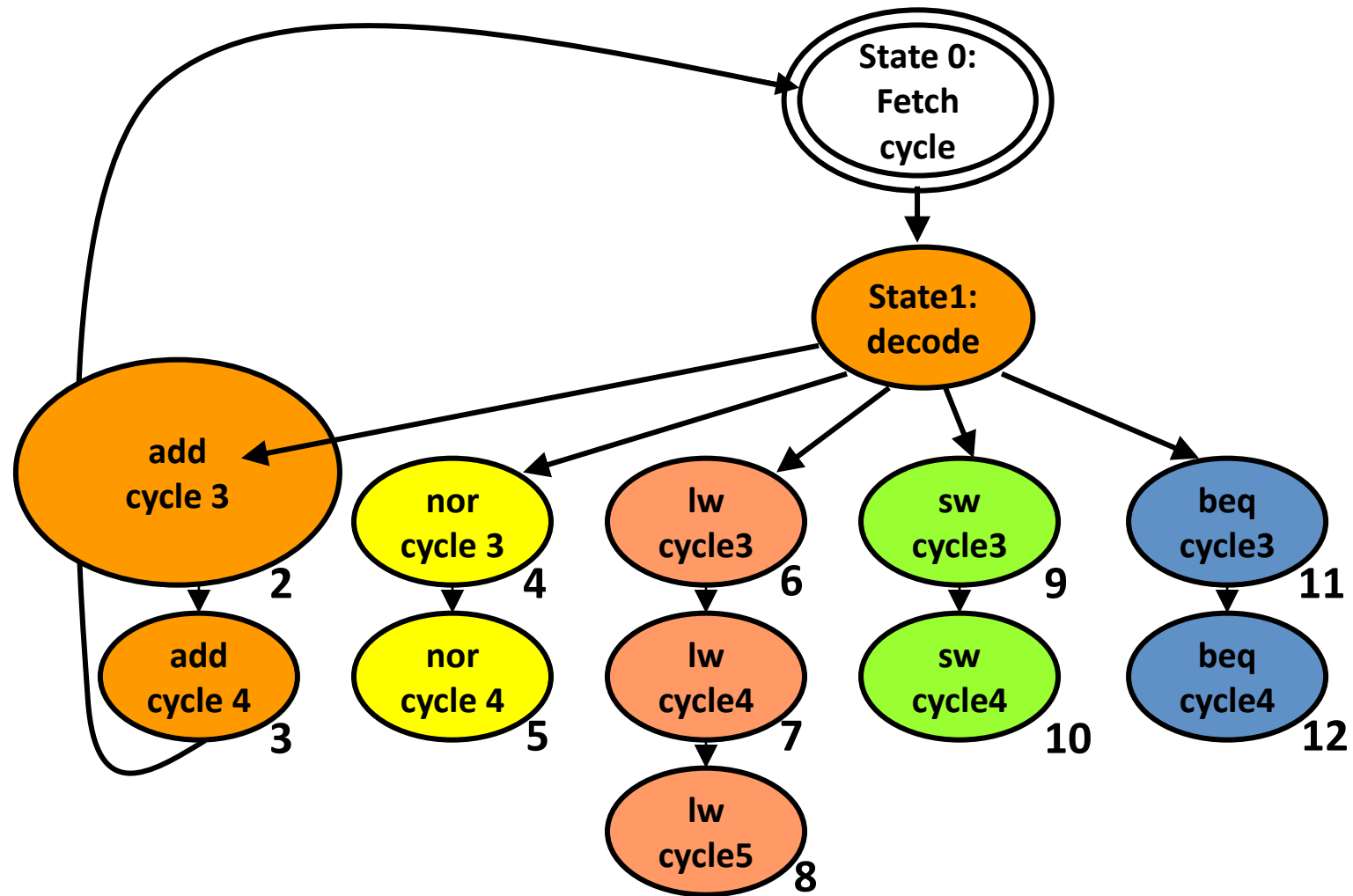


State 2: **Add** Cycle 3 Operation

Send control signals to MUX to select values of regA and regB and control signal to ALU to add

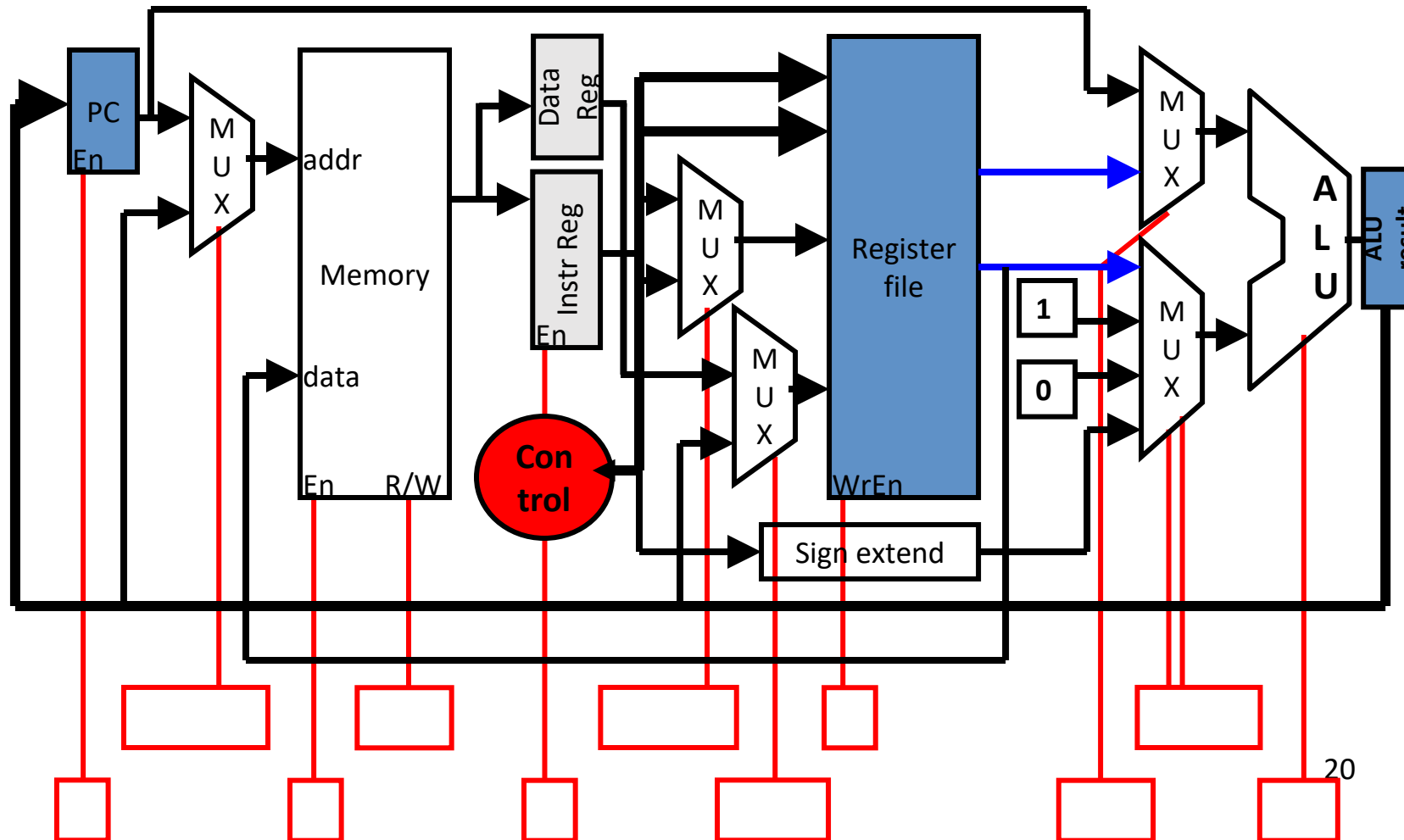


State 2: Add Cycle 3 Operation

Send control signals to MUX to select values of regA and regB and control signal to ALU to add

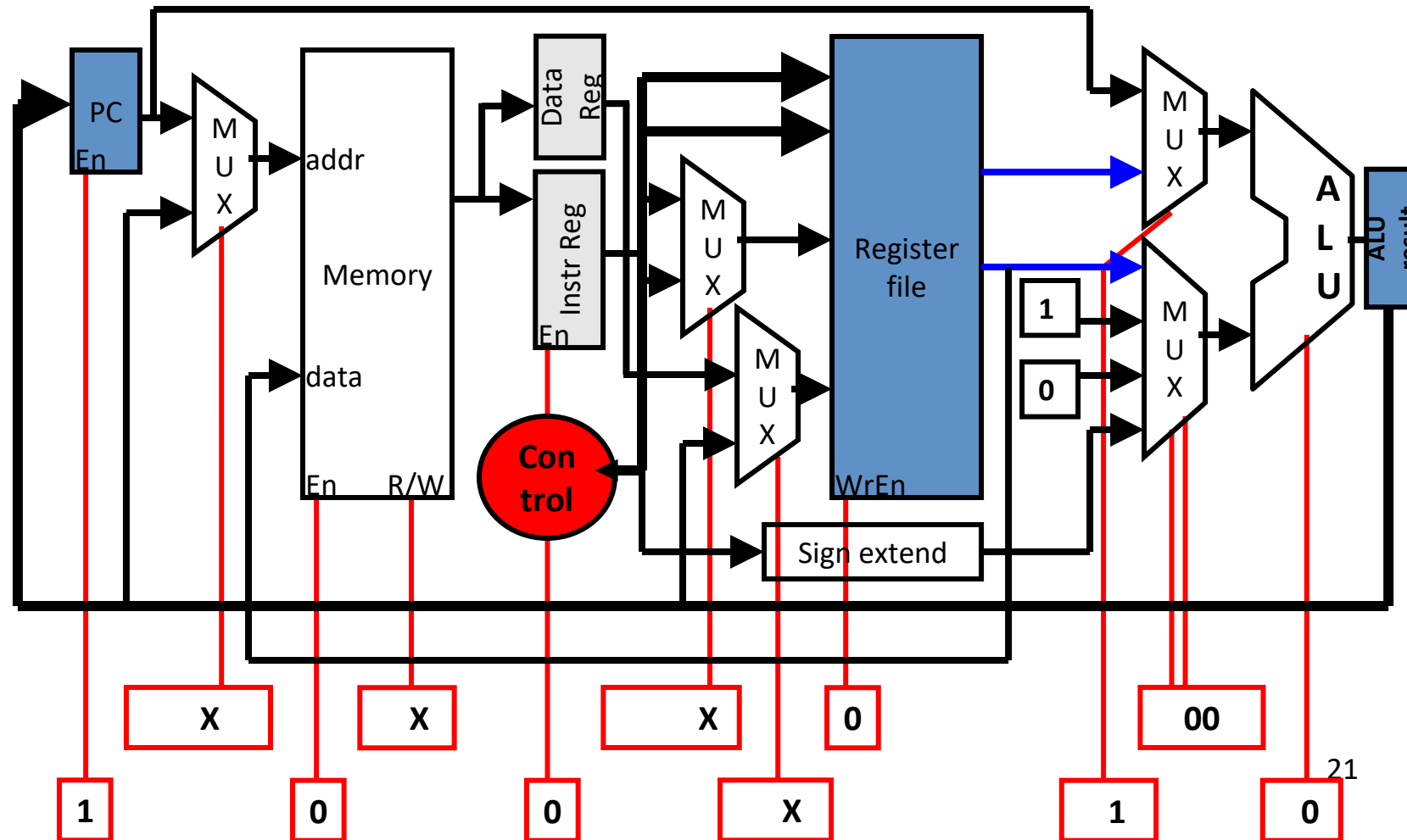


State 3: Add cycle 4

 


Add Cycle 4 (State 3) Operation

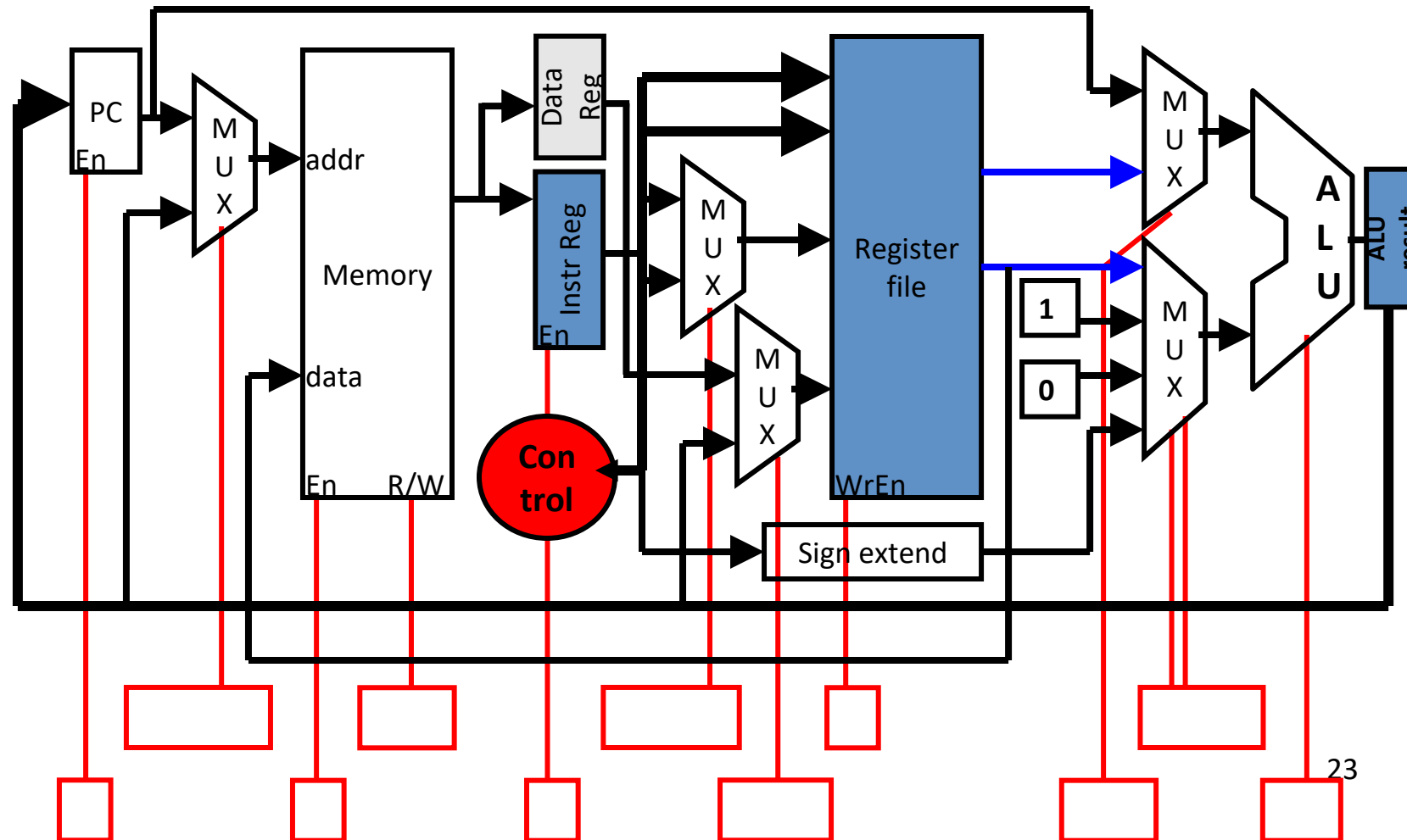Send control signal to address MUX to select dest and to data MUX to select ALU output, then send write enable to register file.




Add Cycle 4 (State 3) Operation

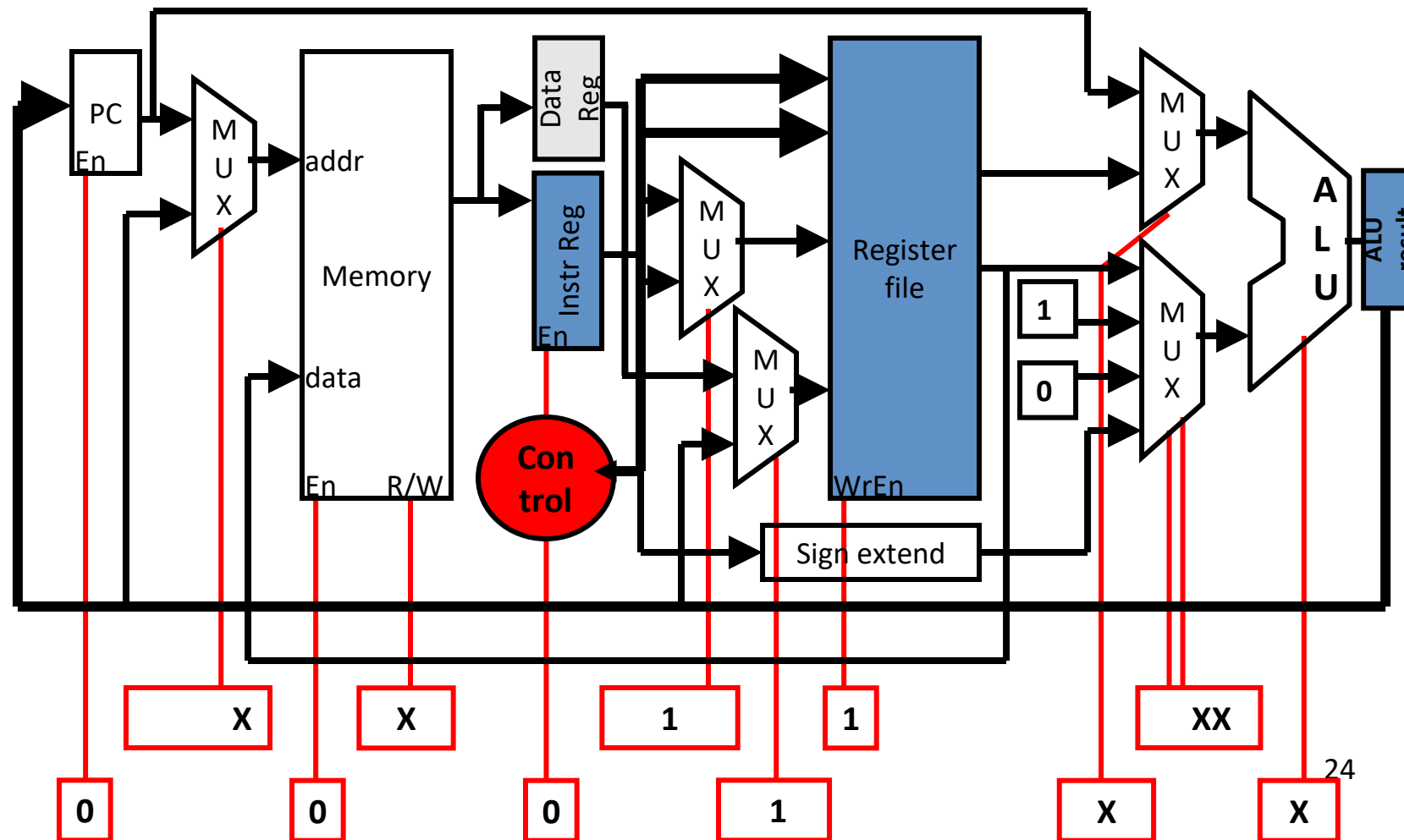
Send control signal to address MUX to select dest and to data MUX to select ALU output, then send write enable to register file.




Building the Control Rom

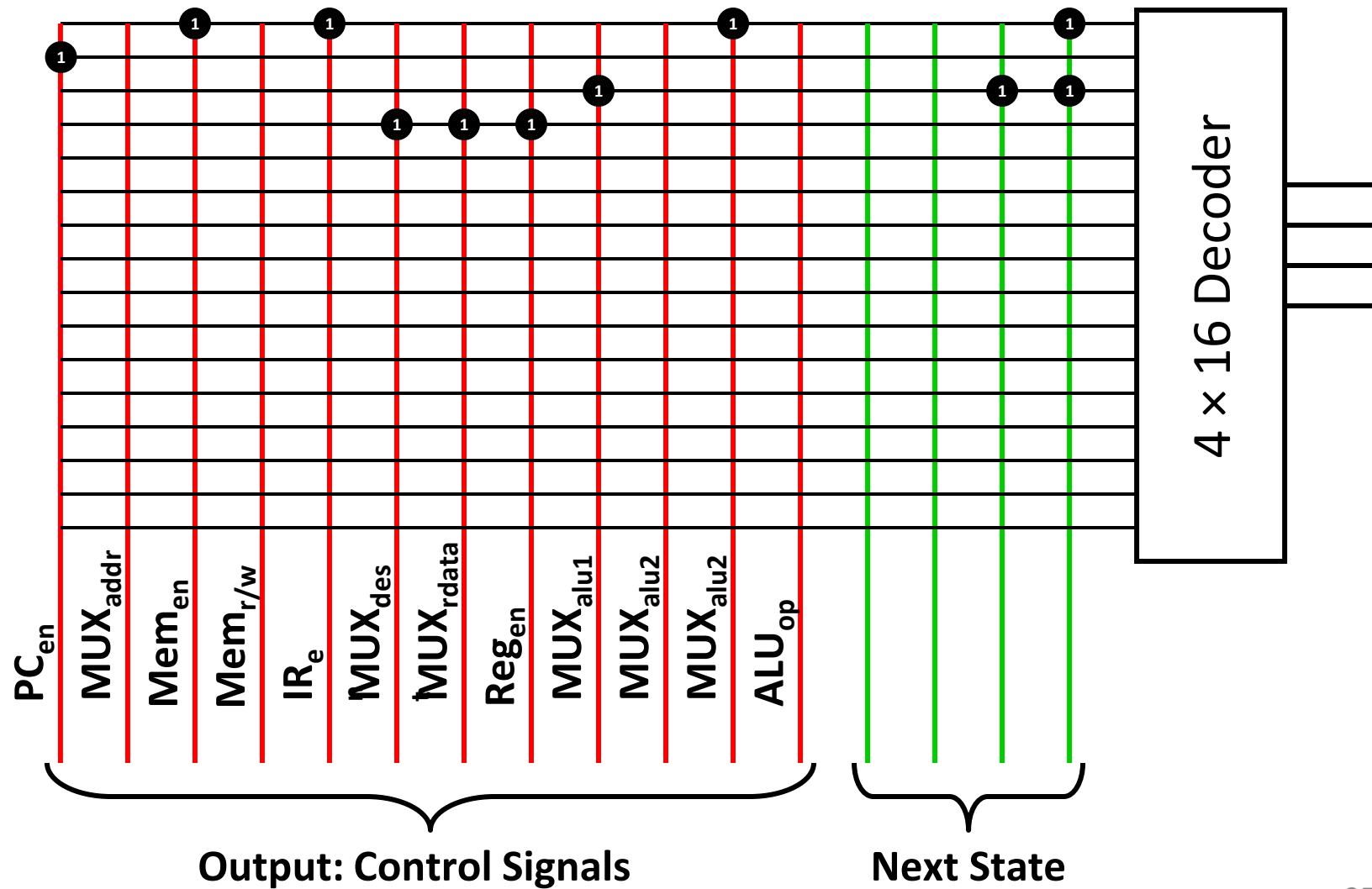

 Return to State 0: Fetch cycle to execute the next instruction




Control Rom for nor (4 and 5)

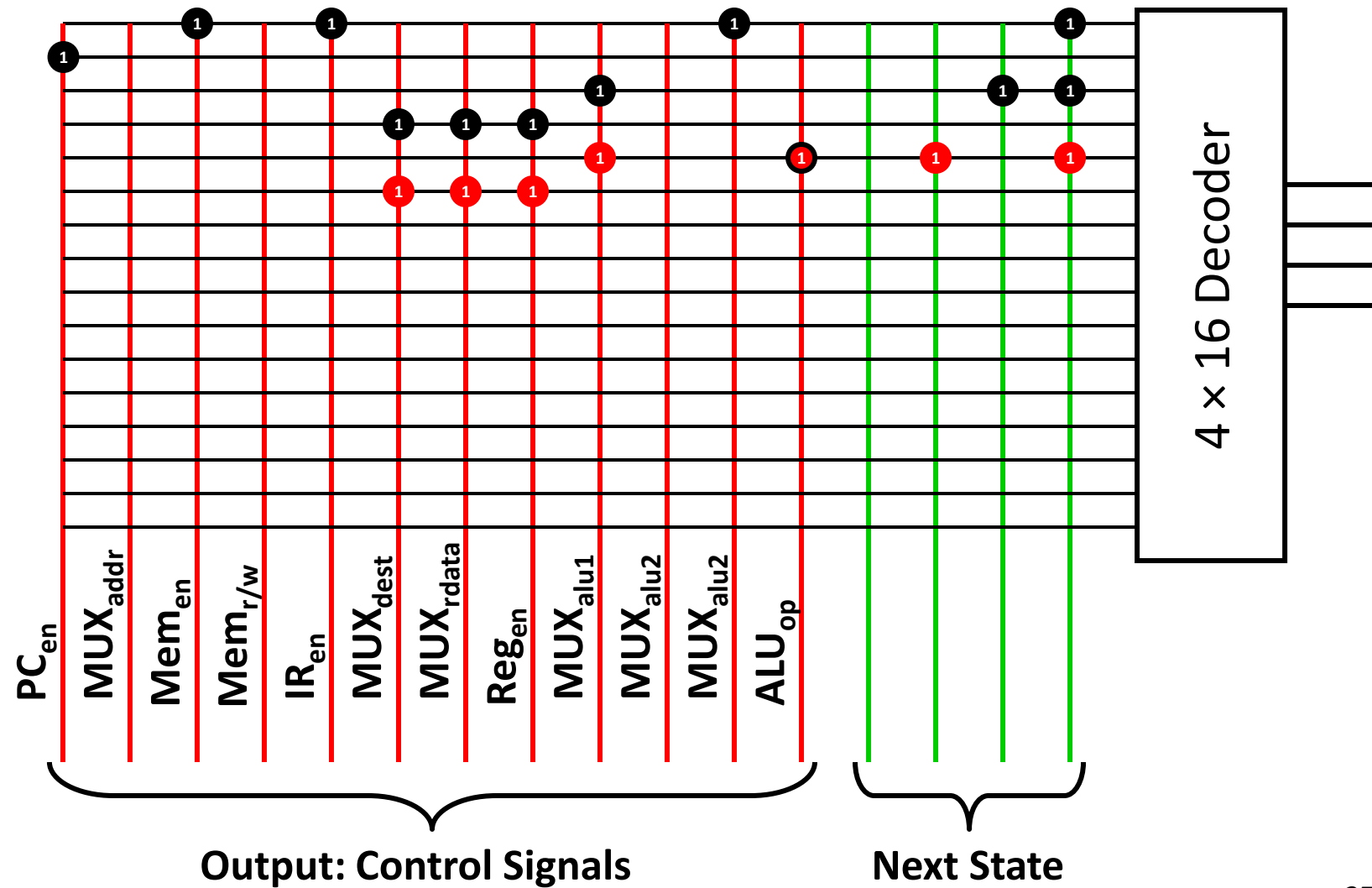


Same output as
add except
 ALU_{op} and Next
State

Return to State 0: Fetch cycle to execute the next instruction

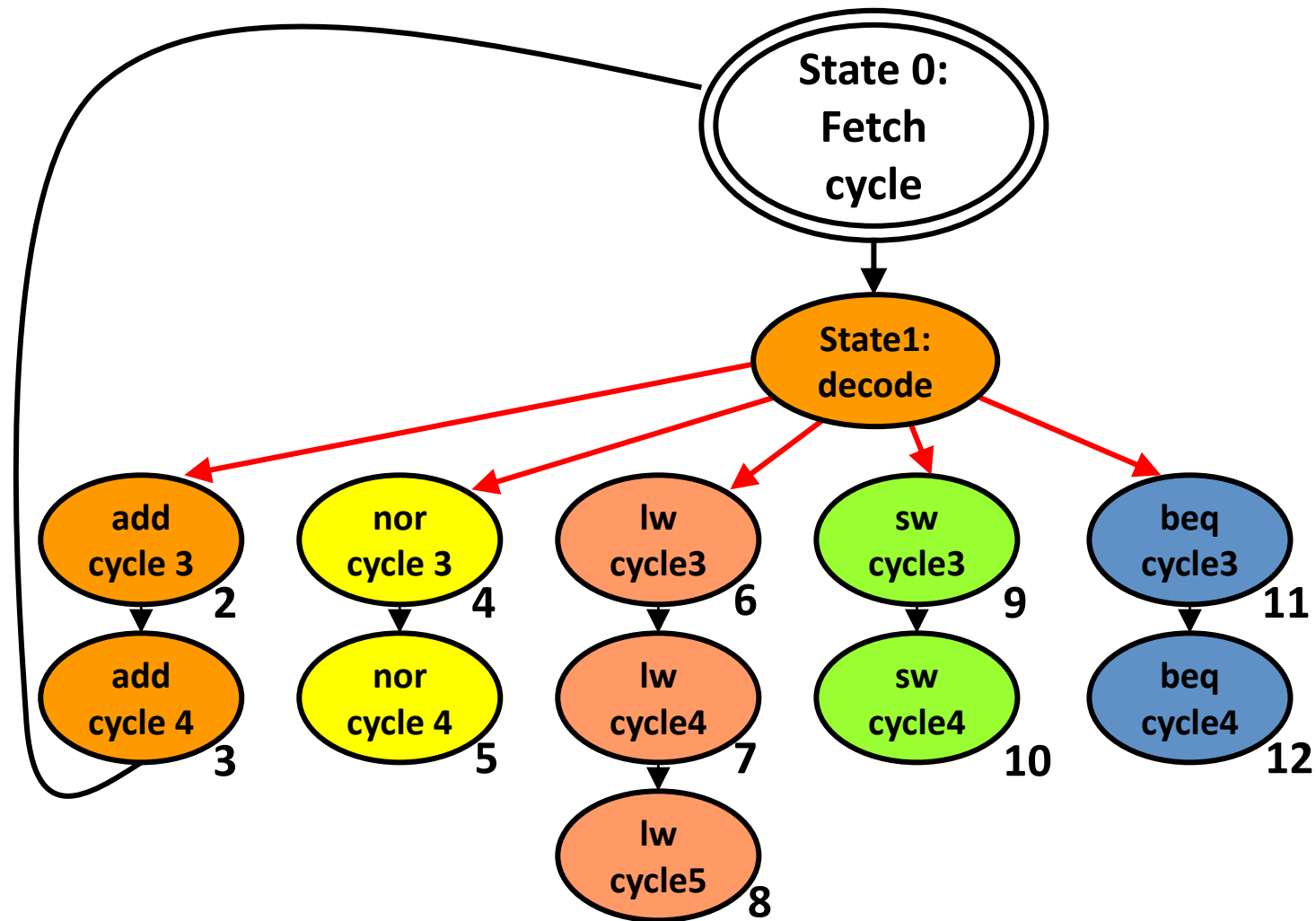


State 6: LW cycle 3

Calculate address for memory reference

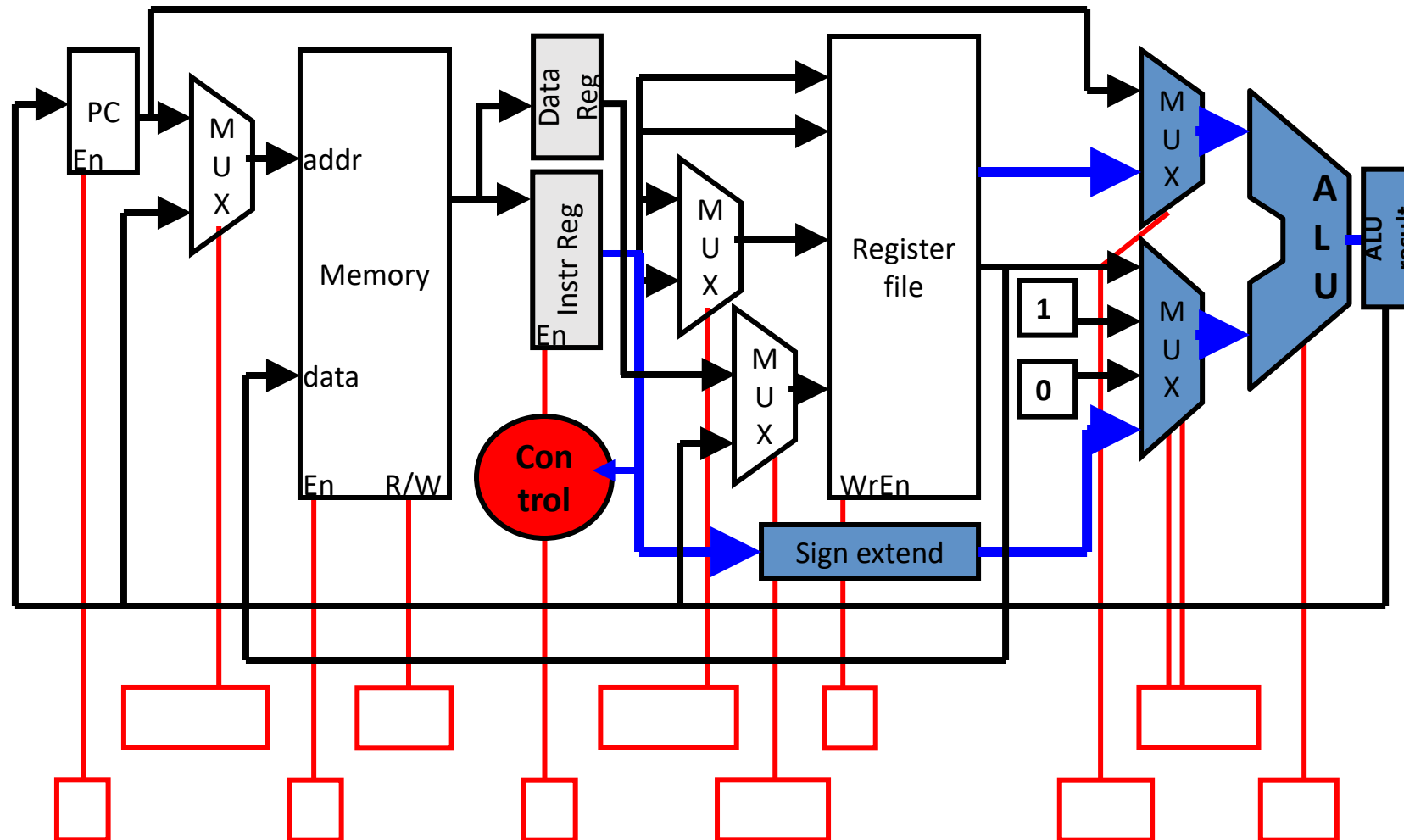


State 6: LW cycle 3


Calculate address for memory reference

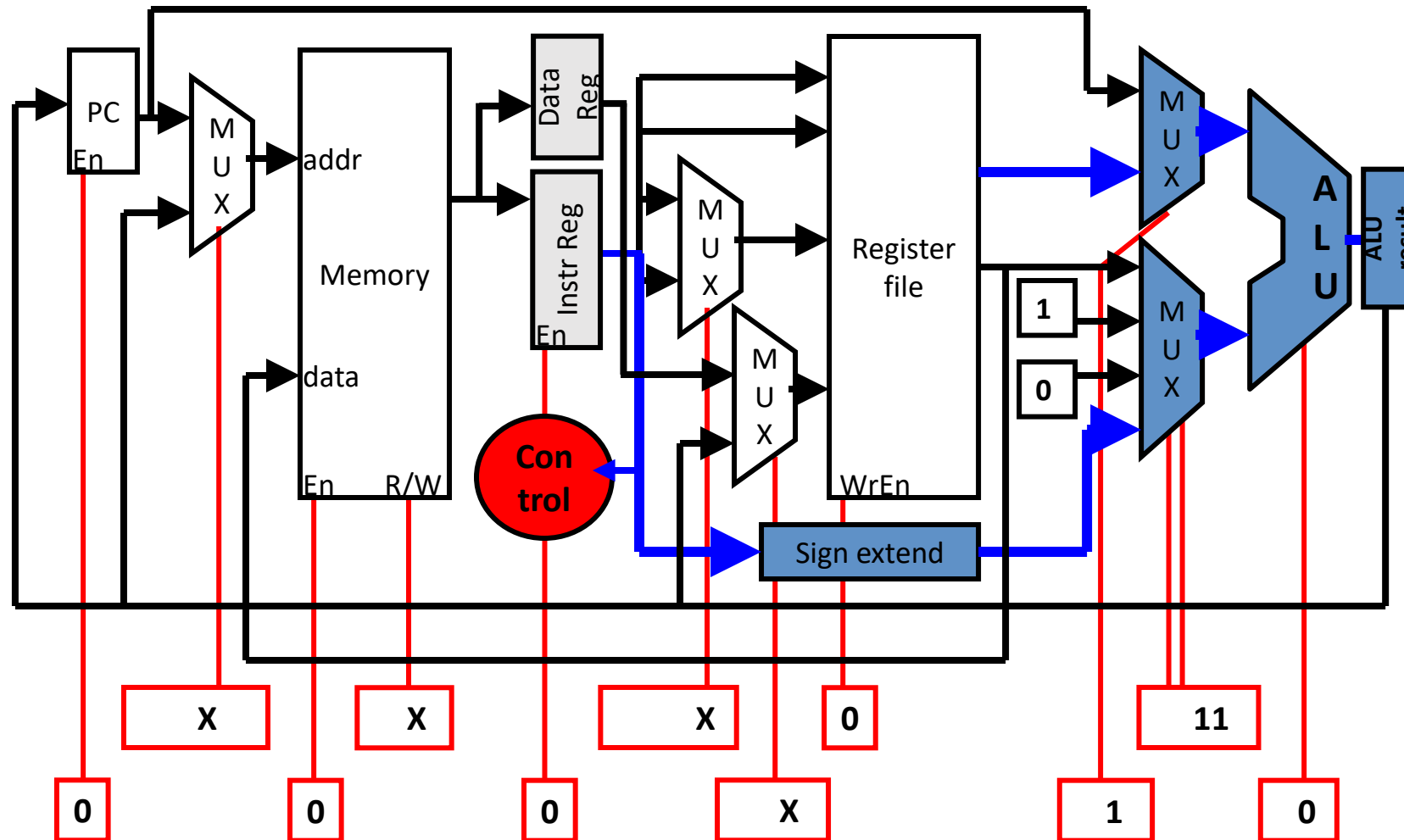


Control Rom (lw cycle 3)

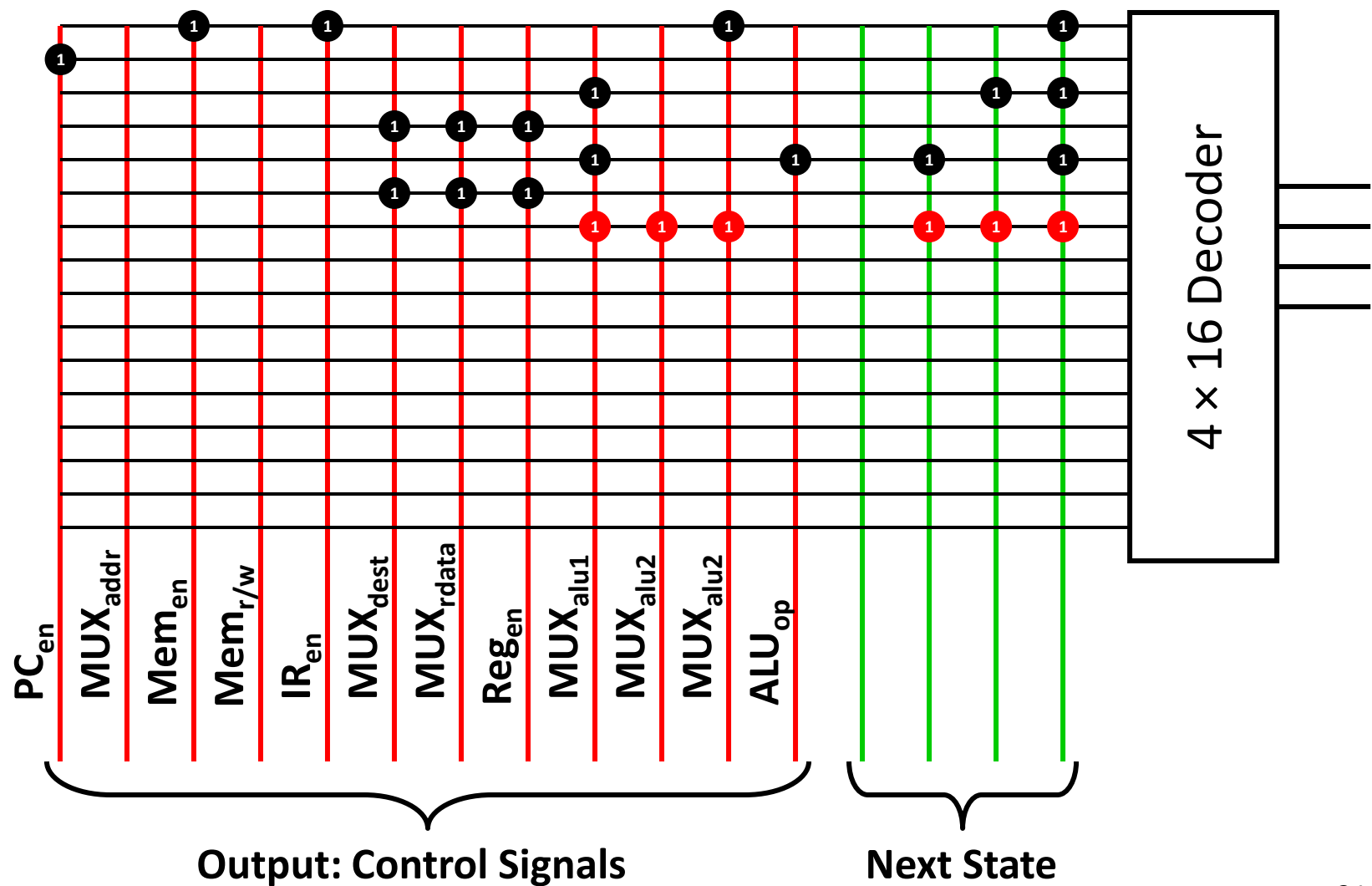


State 7: LW cycle 4

 

State 7: LW cycle 4

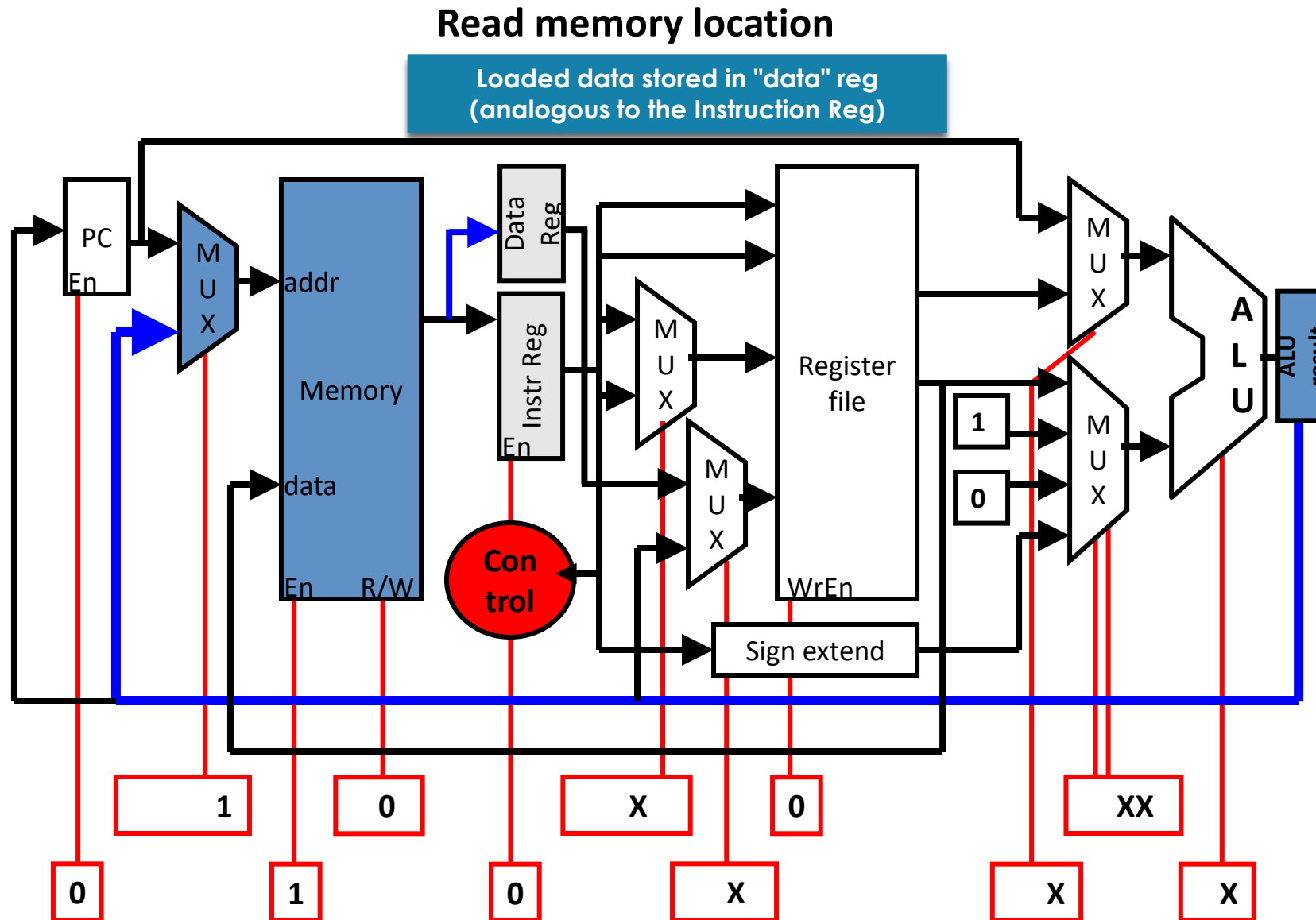


Control Rom (lw cycle 4)

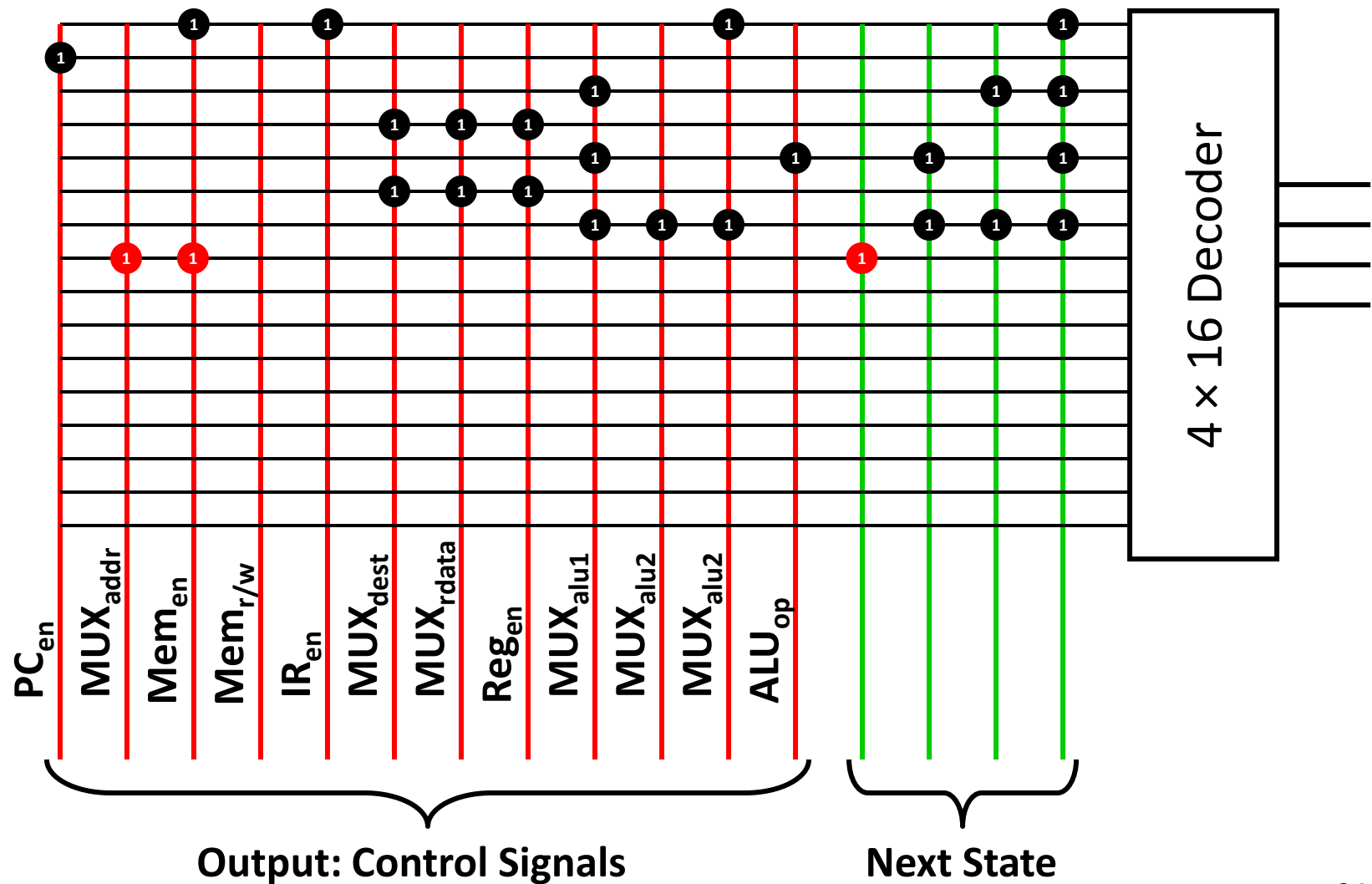


State 8: LW cycle 5

Write memory value to register file

 


State 8: LW cycle 5


Write memory value to register file

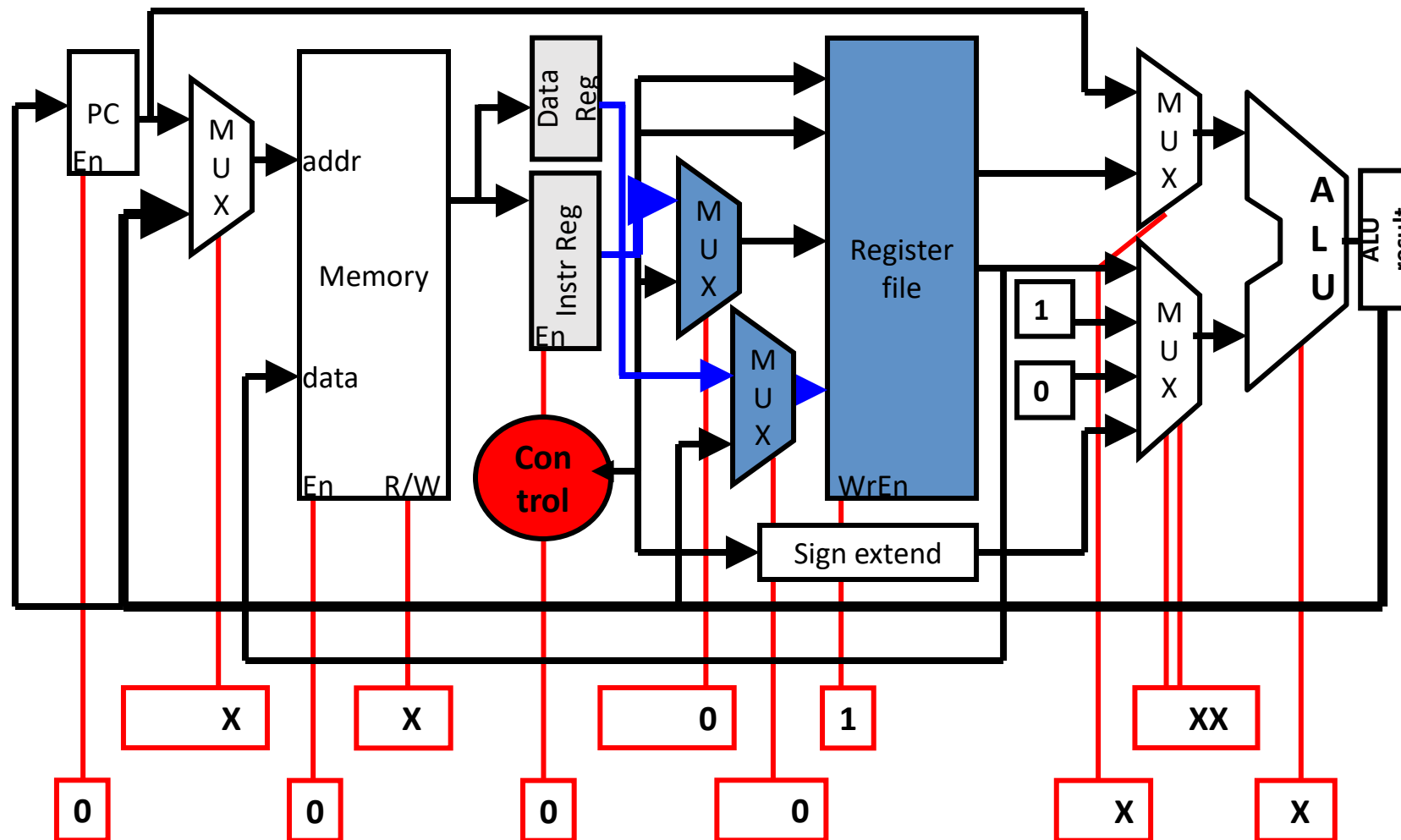

Control Rom (lw cycle 5)

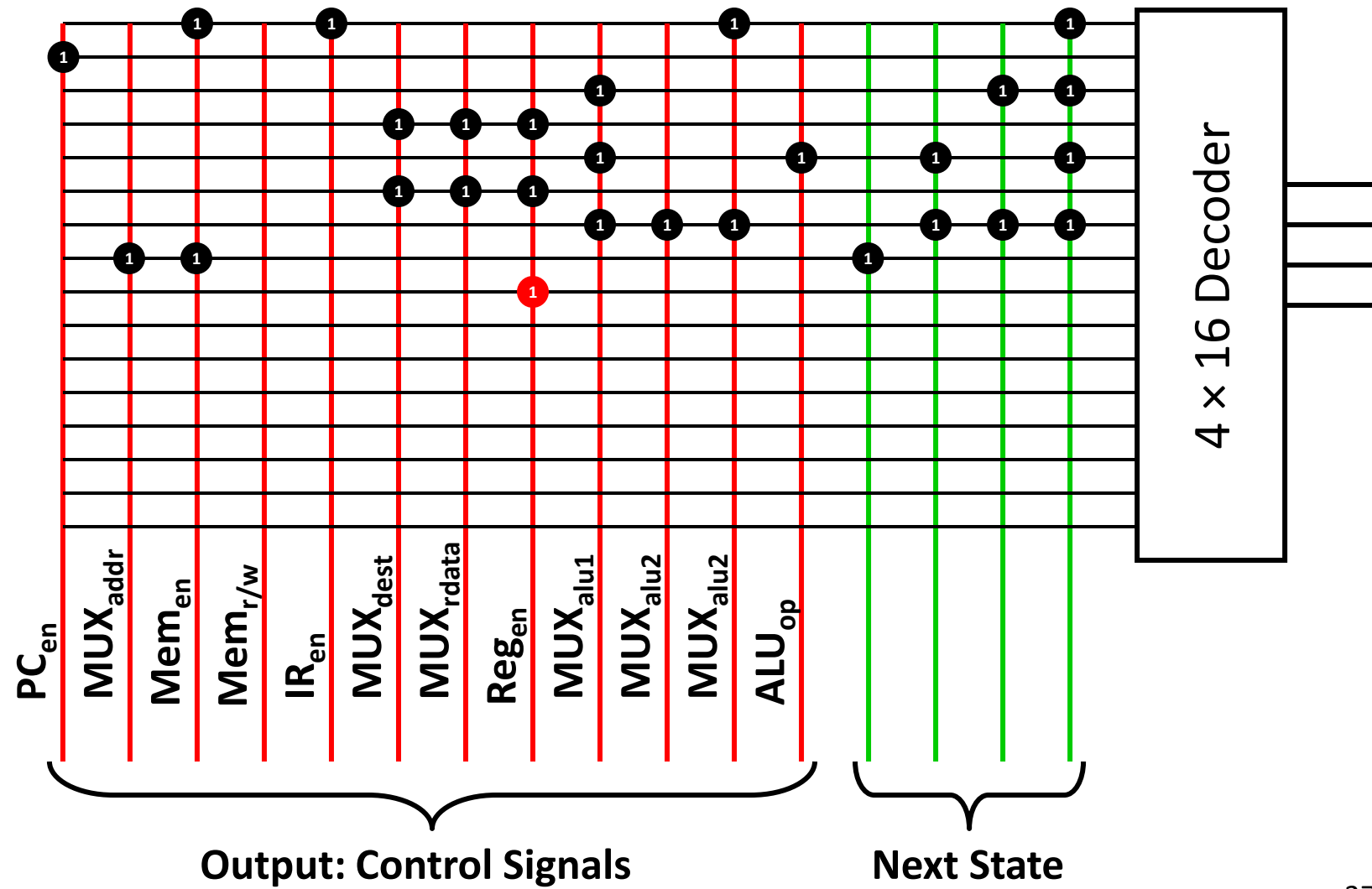


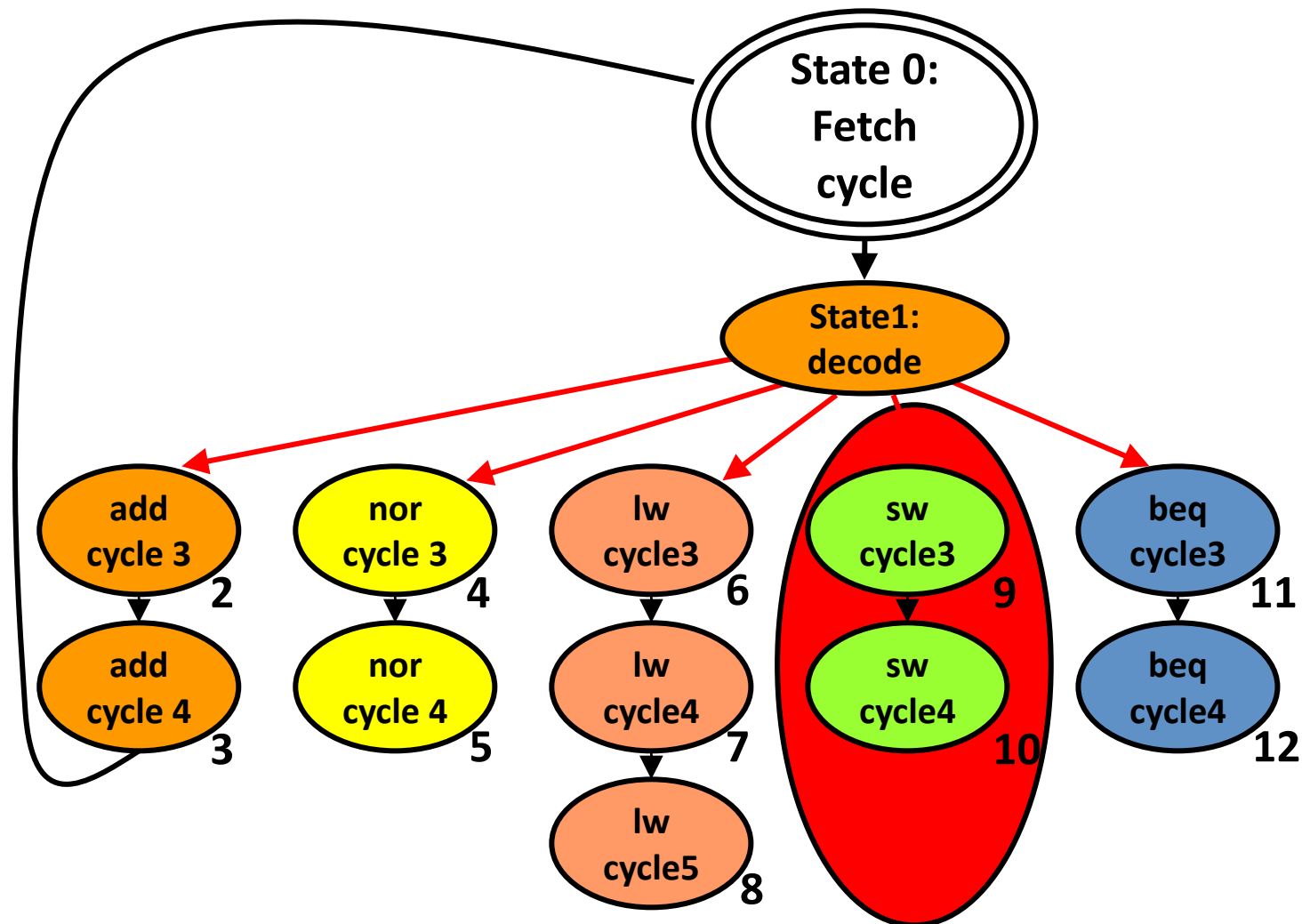Return to State 0: Fetch cycle to execute the next instruction




Same as lw, except $\text{Mem}_{r/w}$ and Next State

Control Rom (sw cycles 3 and 4)

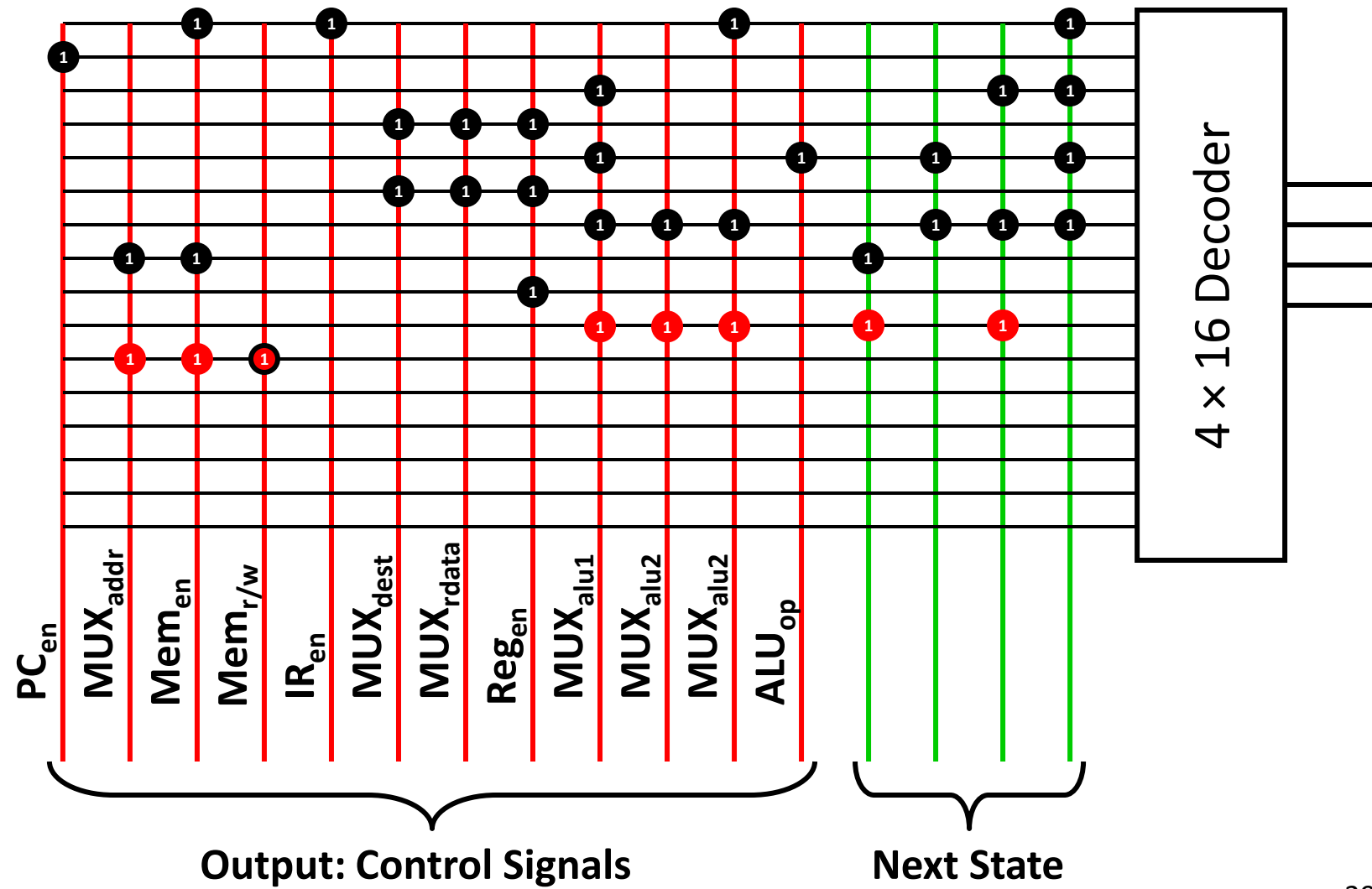


Return to State 0: Fetch cycle to execute the next instruction

 

State 11: beq cycle 3


Poll: What will the control bits be?

Calculate target address for branch

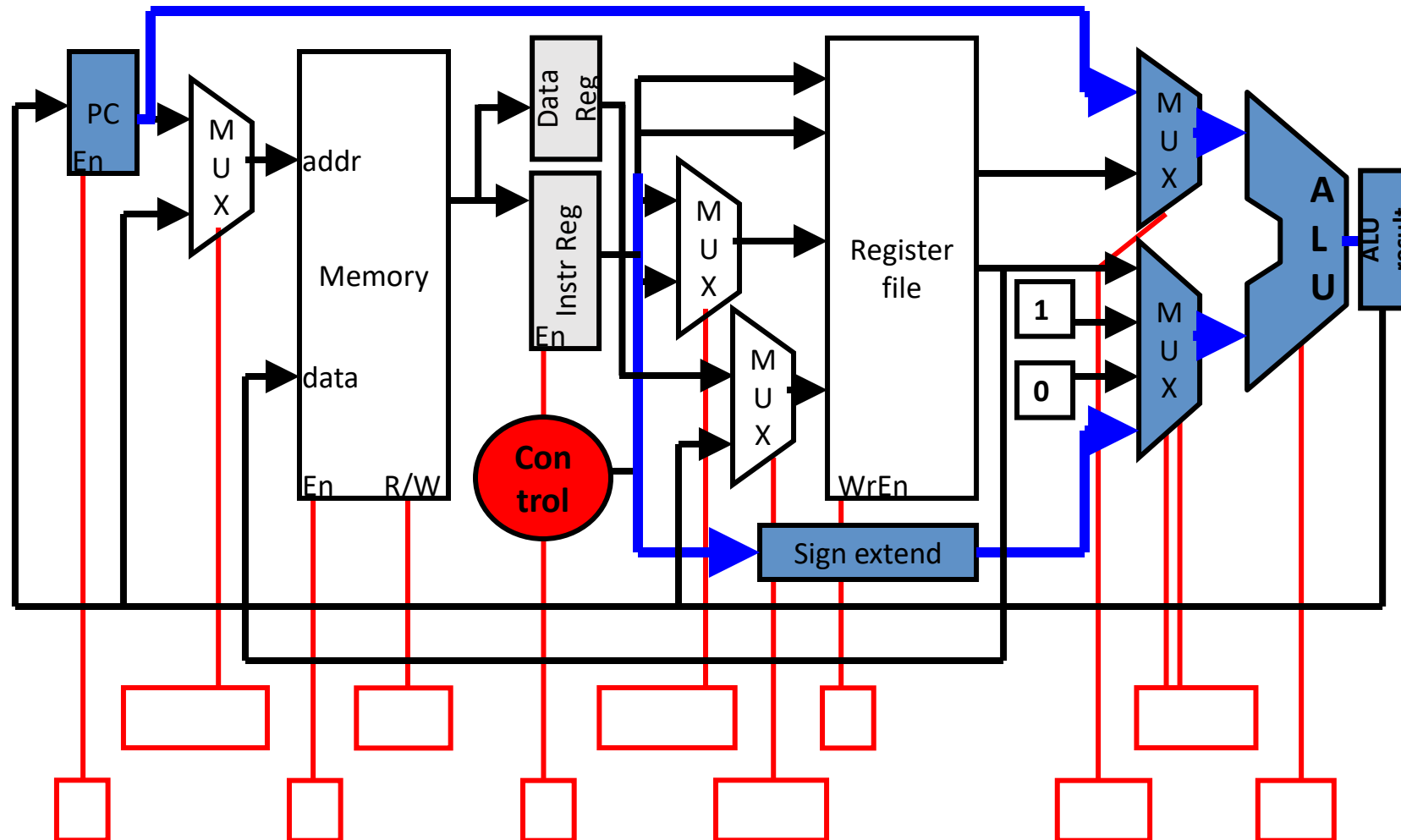


State 11: beq cycle 3

Calculate target address for branch

 


Control Rom (beq cycle 3)

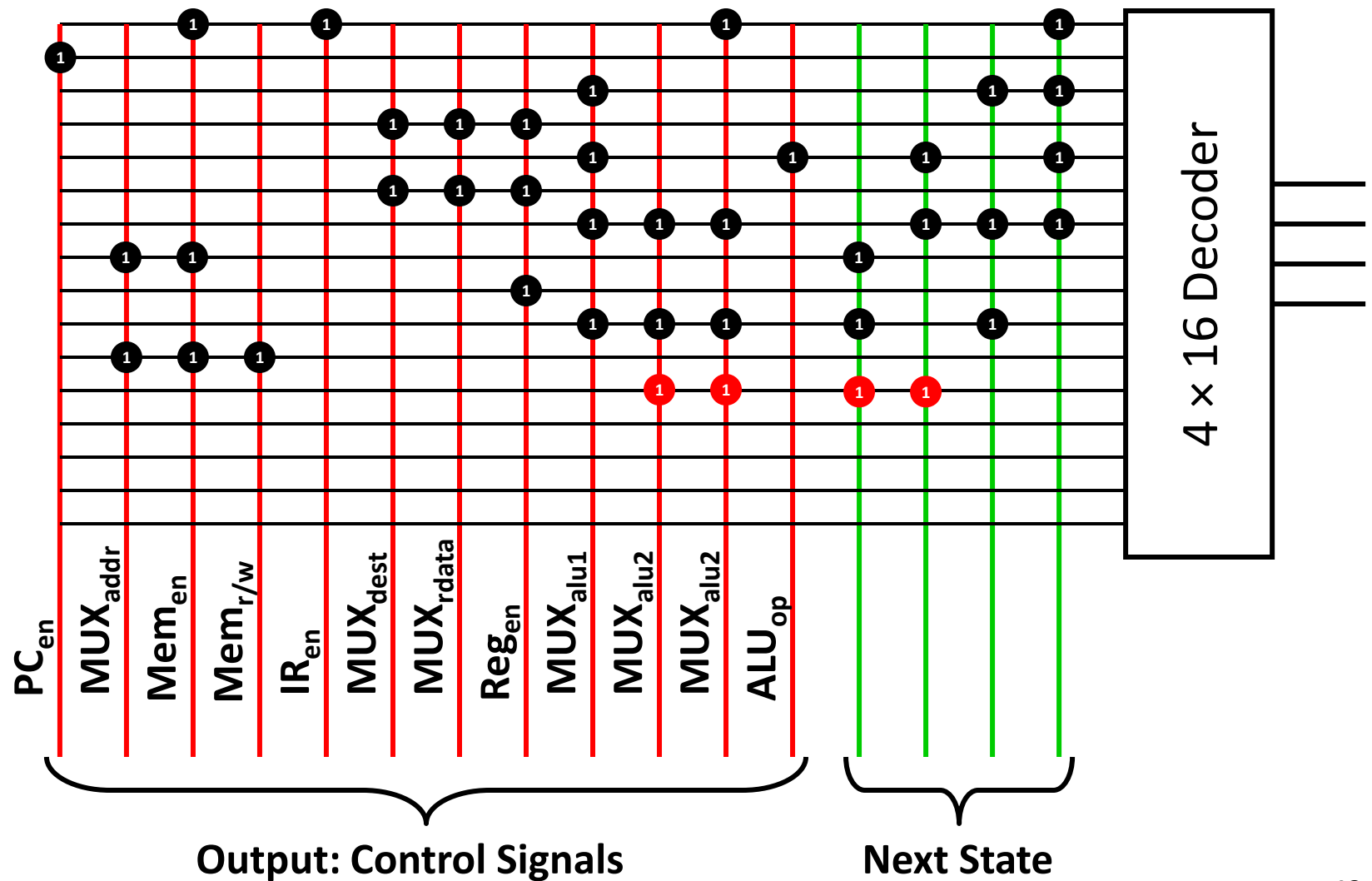


State 12: beq cycle 4

Write target address into PC
if ($\text{data}_{\text{rega}} == \text{data}_{\text{regb}}$)

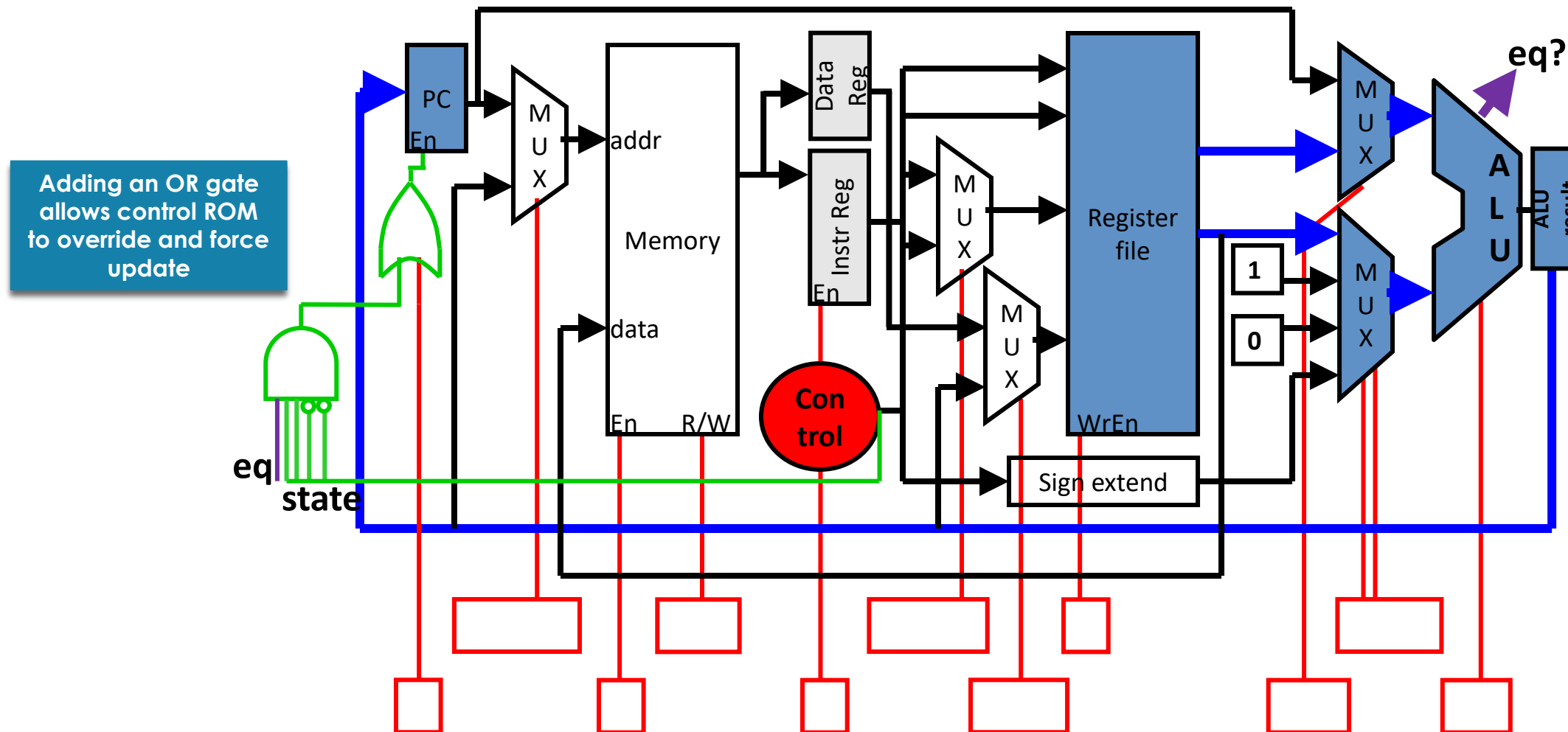


State 12: beq cycle 4

 Write target address into PC
if ($\text{data}_{\text{rega}} == \text{data}_{\text{regb}}$)



Control Rom (beq cycle 4)

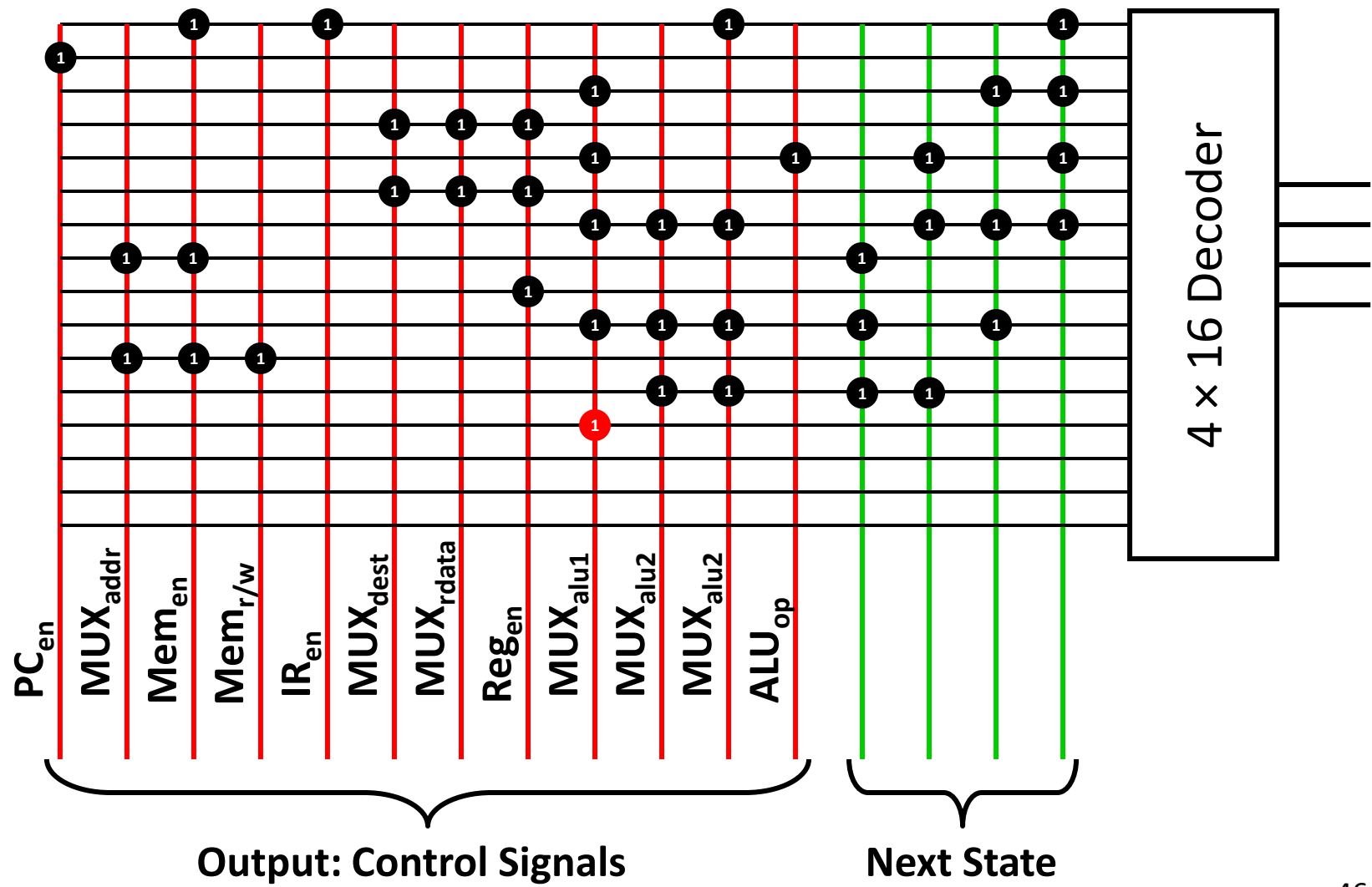

Single vs Multi-cycle Performance

1 ns – Register File read/write time

2 ns – ALU/adder

2 ns – memory access

0 ns – MUX, PC access, sign extend,
ROM

Poll: How many ns does SC take?
MC?

1. Assuming the above delays, what is the best cycle time that the LC2k multi-cycle datapath could achieve? Single cycle?
2. Assuming the above delays, for a program consisting of 25 LW, 10 SW, 45 ADD, and 20 BEQ, which is faster?

Single vs Multi-cycle Performance

1 ns – Register File read/write time

2 ns – ALU/adder

2 ns – memory access

0 ns – MUX, PC access, sign extend,
ROM

1. Assuming the above delays, what is the best cycle time that the LC2k multi-cycle datapath could achieve? Single cycle?

$$\text{MC: } \text{MAX}(2, 1, 2, 2, 1) = 2\text{ns}$$

$$\text{SC: } 2 + 1 + 2 + 2 + 1 = 8\text{ ns}$$

2. Assuming the above delays, for a program consisting of 25 LW, 10 SW, 45 ADD, and 20 BEQ, which is faster?

$$\text{SC: } 100 \text{ cycles} * 8 \text{ ns} = 800 \text{ ns}$$

$$\text{MC: } (25*5 + 10*4 + 45*4 + 20*4) \text{cycles} * 2\text{ns} = 850 \text{ ns}$$



Single and Multi-cycle performance

- Wait, multi-cycle is worse??
- For our ISA, most instructions take about the same time
- Multi-cycle shines when some instructions take much longer
- E.g. if we add a long latency instruction like multiply:
 - Let's say operation takes 10 ns, but could be split into 5 stages of 2 ns
 - SC: clock period = 16 ns, performance is 1600 ns
 - MC: clock period = 2 ns, performance is 850 ns

Performance Metrics – Execution time

- What we really care about in a program is **execution time**
 - **Execution time** = total instructions executed X CPI x clock period
 - The "Iron Law" of performance
- CPI = **average** number of clock **cycles per instruction** *for an application*
- To calculate multi-cycle CPI we need:
 - Cycles necessary for each type of instruction
 - Mix of instructions executed in the application (dynamic instruction execution profile)

Poll: What are the units of
(instructions executed x CPI x
clock period)?


Datapath Summary

- Single-cycle processor
 - CPI = 1 (by definition)
 - clock period = ~ 10 ns
- Multi-cycle processor
 - CPI = ~ 4.25
 - clock period = ~ 2 ns
- Better design:
 - CPI = 1
 - clock period = ~ 2 ns
- How??
 - Work on multiple instructions at the same time


Pipelining

- Want to execute an instruction?
 - Build a processor (multi-cycle)
 - Find instructions
 - Line up instructions (1, 2, 3, ...)
 - Overlap execution
 - Cycle #1: Fetch 1
 - Cycle #2: Decode 1 Fetch 2
 - Cycle #3: ALU 1 Decode 2 Fetch 3
 -
 - This is called pipelining instruction execution.
 - Used extensively for the first time on IBM 360 (1960s).
 - CPI approaches 1.

Pipelining

 

Pipelining

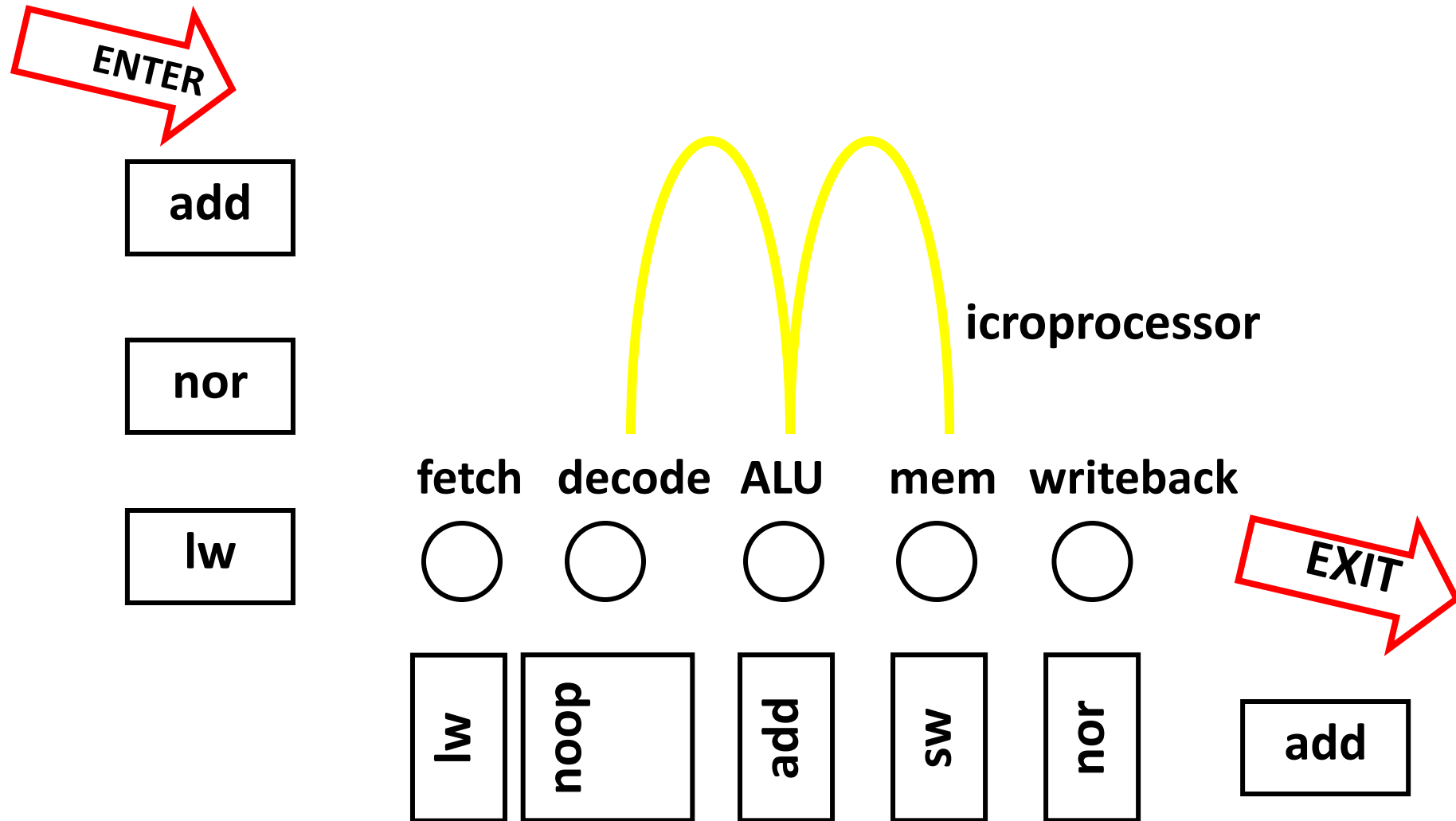


Pipelined implementation of LC2K

- Break the execution of the instruction into cycles.
 - Similar to the multi-cycle datapath
- Design a separate datapath **stage** for the execution performed during each cycle.
 - Build **pipeline registers** to communicate between the stages.
 - Whatever is on the left gets written onto the right during the next cycle
 - Kinda like the **Instruction Register** in our multi-cycle design, but we'll need one for each stage



Our new pipelined datapath

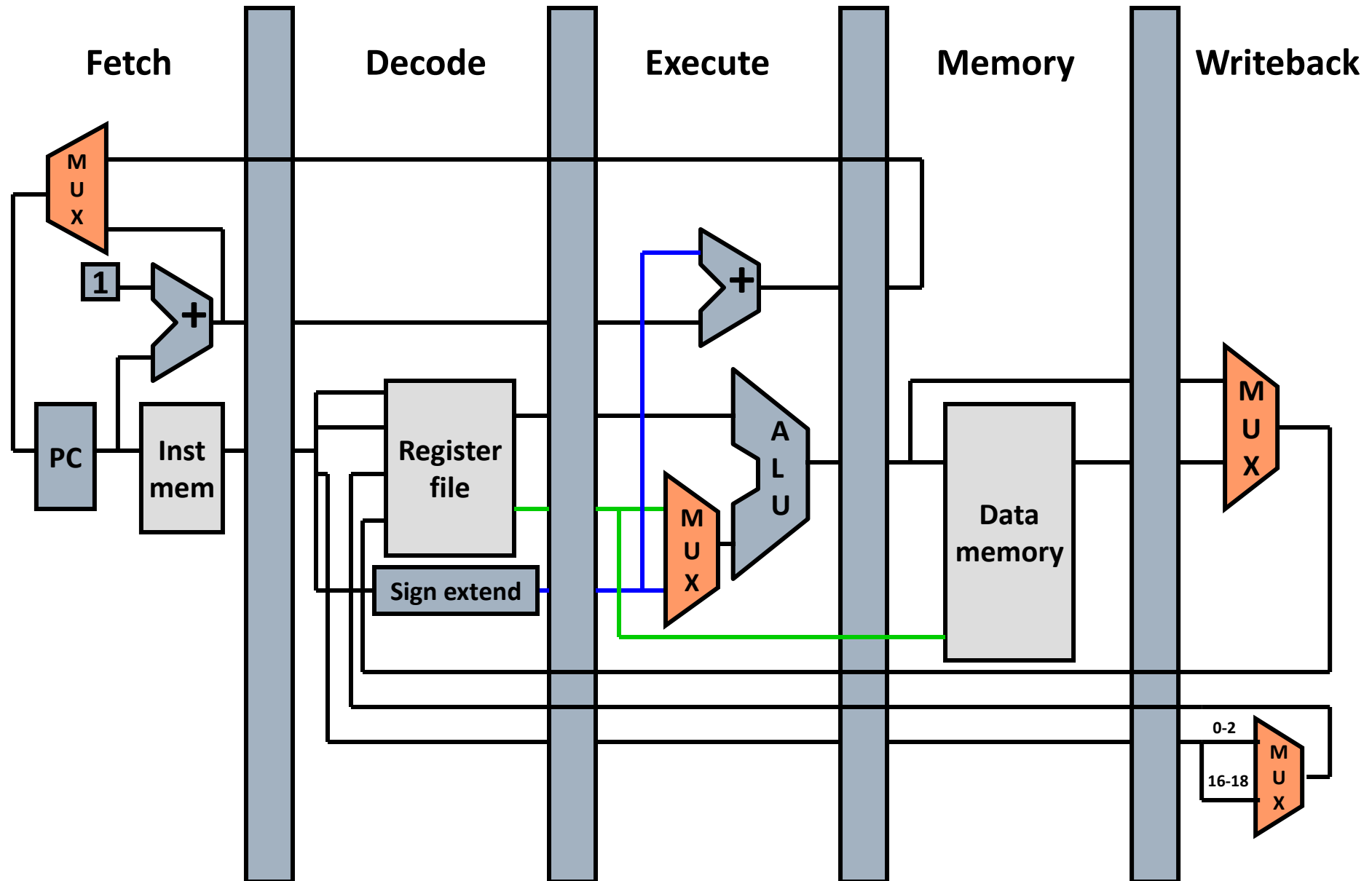

Next time

- More pipelining